


#### SPECIFIC INSTRUCTIONS

- You must answer the 20 questions so as to be able to obtain the maximum score.
- All of the blank pages on the back of this topic can be used for drafting if you wish. No draft will be distributed to you.
- The use of the non-programmable calculator is authorized
- In order to eliminate random answer strategies, each correct answer is rewarded with 3 points, while each wrong answer is penalized by the withdrawal of 1 point.
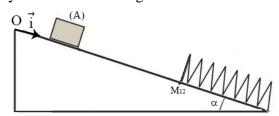
### First exercise: Mechanical energy

We propose to determine the variation of the mechanical energy of a system between two given instants.

We have a table inclined by  $15^\circ$  with respect to the horizontal. During its motion, at an instant t, the mobile (A), a point mass of mass m=220 g, undergoes forces due to friction whose resultant  $\vec{f}=-f\vec{1}$  is constant and in the opposite direction to  $\vec{V}=V\vec{1}$  (V>0), the velocity of the center of mass M of (A) with respect to an axis (O,  $\vec{1}$ ) parallel to the line of greatest slope. An appropriate device records, at equal intervals of time to  $\tau=40$  ms, the abscissa



x of M and the value of V. The measurements are registered in the table below. (Take:  $g = 10 \text{ m/s}^2$ ).

Instant	$t_0$	$t_1$	$t_2$	t <sub>3</sub>	<b>t</b> 4	<b>t</b> <sub>5</sub>	$t_6$	t <sub>7</sub>	t <sub>8</sub>	t <sub>9</sub>	$t_{10}$	t <sub>11</sub>	t <sub>12</sub>
Position	$\mathbf{M}_0$	$\mathbf{M}_1$	$M_2$	<b>M</b> <sub>3</sub>	$M_4$	$M_5$	$M_6$	$M_7$	$M_8$	M <sub>9</sub>	$M_{10}$	$M_{11}$	$M_{12}$
Abscissa x(m)	0.000	0.012	0.027	0.047	0.070	0.097	0.128	0.163	0.201	0.244	0.290	0.341	0.395
V(m/s)	0.242	0.338	0.435	0.532	0.629	0.726	0.823	0.919	1.016	1.113	1.210	1.307	1.403

- 1. Let P be the algebraic measurement of the linear momentum of (A) at an instant t. The instantaneous variation of the linear momentum,  $\Delta \vec{P} = \Delta P \vec{i}$ , is supposed to be constant;  $\Delta P$ , at the instant  $t_6$ , is equal to:
- **a)**  $\Delta P = 0.0313$  kg. m/s;
- **b)**  $\Delta P = 0.0531 \text{ kg .m/s};$
- c)  $\Delta P = 0.0425 \text{ kg .m/s}.$
- **2.** By applying Newton's second law  $(\vec{F} = \frac{d\vec{P}}{dt})$ , the value of F is:
- **a)** F = 0.665 N;
- **b**) F = 0.531 N;
- **c)** F = 0.426 N.
- **3.** The value N of the normal reaction  $\overrightarrow{N}$  of the inclined support on (A) is equal to:
- a) N = 2.125 N;
- **b)** N = 1.569 N;
- **c**) N = 0.589 N.
- **4.** The algebraic measurement F of the resultant  $\vec{F}$  of the forces exerted on (A) is expressed by:
- a) F = 0.608 f;
- **b**) F= 0.569 f;
- **c**) F = 0.508 + f.

- **5.** The value of f is then:
- **a)** f = 0.021 N;
- **b**) f = 0.038 N;
- **c)** f = 0.058 N.
- **6.** The work  $W(\vec{f})$  done by  $\vec{f}$  between the points  $M_0$  and  $M_{12}$  is equal to:
- **a)**  $W(\vec{f}) = -0.023 J;$
- **b**)  $\vec{W(f)} = -0.008 \text{ J};$
- c)  $W(\vec{f}) = -0.015 J.$
- 7. Knowing that the horizontal plane passing through  $M_{12}$  is chosen as the reference level for the gravitational potential energy, the mechanical energy of the system (mobile Earth) at the instant  $t_{12}$  is equal to:
- **a)** ME  $(t_{12}) = 0.184$  J;
- **b)** ME  $(t_{12}) = 0.126 \text{ J};$
- **c)** ME  $(t_{12}) = 0.217$  J.
- **8.** At the point  $M_{12}$ , the mobile (A) hits a spring, of negligible mass and of stiffness constant k. The maximum compression of the spring is of 10 cm. Let C be the point reached then by (A).
- **8.1.** The mechanical energy ME of the system ((A), spring, Earth) at point (C) is expressed by:
- a) ME(C) = 0.005k + 0.00569 (ME in J);
- **b)** ME(C) = 0.005k 0.0569 (ME in J);
- c) ME(C) = 0.05k 0.569 (ME in J).
- **8.2.** The work  $W(\vec{f})$  done by  $\vec{f}$  between the points  $M_{12}$  and C is equal to :
- **a)**  $W(\vec{f}) = -0.0021 J;$
- **b**)  $W(\vec{f}) = -0.0058 J;$
- **c**)  $W(\vec{f}) = -0.0038 J.$
- **8.3.** The stiffness constant k of the spring is equal to :
- **a)** k = 54.0 N/m;
- **b)** k = 31.5 N/m;
- c) k = 42.3 N/m.

#### Second exercise: Role of a coil in a circuit

The circuit shown in figure 1 is carried out where:

- (G) is an ideal generator of emf E = 9 V;
- (D<sub>1</sub>) is a resistor of resistance  $R_1 = 90 \Omega$ ;
- $(D_2)$  is a resistor of resistance  $R_2$ ;
- (B) is a coil of inductance L = 1 H and of negligible resistance;
- (K) is a special switch causing no loss of energy when it passes from position 1 to position 2.

# 

## A- Current growth in the circuit (R<sub>1</sub>L)

The switch is placed in position 1 at an instant chosen as the origin of the times ( $t_0 = 0$ ). At an instant t, the circuit carries a current  $i_1$ .

**1.** The differential equation in  $i_1$  is:

**a**) 
$$E = R_1 \frac{di_1}{dt} + L i_1;$$
  
**b**)  $0 = L \frac{di_1}{dt} + R_1 i_1;$ 

**b)** 
$$0 = L \frac{di_1}{dt} + R_1 i_1;$$

$$\mathbf{c)} E = R_1 i_1 + L \frac{di_1}{dt}.$$

**2.** The solution of the previous differential equation is given by:

**a)** 
$$i_1 = 0.1 (1 - e^{-90.t})$$
 ( $i_1$  in A and t in s);

**b**) 
$$i_1 = 9 (1 - e^{-90.t})$$
 ( $i_1$  in A and t in s);

c) 
$$i_1 = 9 (1 - e^{-0.011.t})$$
 ( $i_1$  in A and t in s).

**3.** In steady state, the value of the current  $i_1$  is:

**a**) 
$$i_1 = 10 A$$
;

**b)** 
$$i_1 = 9 A$$
;

**c**) 
$$i_1 = 0.1 A$$
.

**4.** In steady state, the magnetic energy W<sub>m</sub> stored by the coil is:

**a)** 
$$W_m = 50 J$$
;

**b**) 
$$W_m = 45 J$$
;

**c)** 
$$W_m = 5 \times 10^{-3} \text{ J.}$$

## B - Current decay in the dipole (R<sub>2</sub>L) and lighting of a lamp

## 1. Current decay in the circuit (R<sub>2</sub>L)

At an instant chosen as a new origin of the times  $(t_0 = 0)$ , the switch (K) passes from position 1 to position 2. At an instant t, the circuit carries then a current i<sub>2</sub>.

**1.1.** The differential equation in  $i_2$  is:

a) 
$$L \frac{di_2}{dt} + (R_1 + R_2)i_2 = 0;$$
  
b)  $L \frac{di_2}{dt} + R_2i_2 = 0;$ 

**b)** 
$$L \frac{di_2}{dt} + R_2 i_2 = 0$$


**c**) 
$$L \frac{di_2}{dt} + R_2 i_2 = \frac{E}{R_2}$$
.

**1.2.** The solution of this differential equation is of the form:

**a**) 
$$i_2 = \frac{E}{R_1} e^{-\frac{R_2}{L}t};$$

**b**) 
$$i_2 = \frac{E}{R_2} e^{-\frac{R_2}{L}t};$$

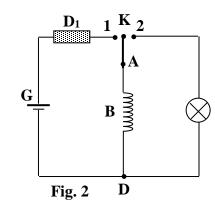**c**) 
$$i_2 = \frac{E}{R_1} e^{-\frac{L}{R_2}t}$$
.



# 2. Duration of lighting of a lamp

The resistor  $D_2$  is a lamp of resistance  $R_2 = 400 \Omega$  (Fig. 2).

This lamp stays on as long as it carries a current that is at least equal to 20 mA. The maximum duration of the lighting the lamp is:


a) 
$$\Delta t = 2 \text{ ms}$$
;

**b**) 
$$\Delta t = 4$$
 ms;


c) 
$$\Delta t = 1$$
 ms.
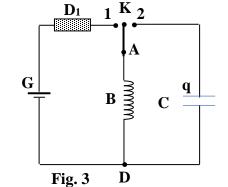
### C – Oscillating circuit

The resistor  $(D_2)$  is replaced by a capacitor of capacitance C (Fig. 3). The switch, placed in position 1, the circuit reaches the steady state. At an instant chosen as the origin of time  $(t_0=0)$ , the switch (K) passes from position 1 to position 2. Using a suitable device, we record the variations of the voltage  $u_C$  across the capacitor and we obtain the waveform of figure 4.



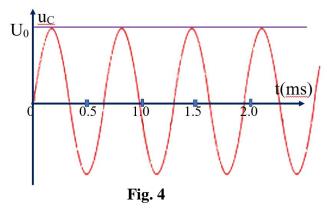- **1.** The proper period  $T_0$  of the oscillations of the LC circuit is:
- **a)**  $T_0 = 1.25 \text{ ms};$
- **b)**  $T_0 = 0.63 \text{ ms};$
- **c**)  $T_0 = 0.5$  ms.
- **2.** The value of the capacitance C of the capacitor is:
- **a**) C = 10 nF;
- **b**)  $C = 10 \mu F$ ;
- **c**) C = 10 mF.
- **3.** The maximum value  $U_0$  of the voltage  $u_C$  across the capacitor is:
- **a**)  $U_0 = 9 V$ ;
- **b**)  $U_0 = 100 \text{ V}$ ;
- **c)**  $U_0 = 1000 \text{ V}.$



# **Solution**

#### SPECIFIC INSTRUCTIONS

- You must answer the 20 questions so as to be able to obtain the maximum score.
- All of the blank pages on the back of this topic can be used for drafting if you wish. No draft will be distributed to you.
- The use of the non-programmable calculator is authorized
- In order to eliminate random answer strategies, each correct answer is rewarded with 3 points, while each wrong answer is penalized by the withdrawal of 1 point.

First exercie: Mechanical energy

First exercie: Mechanical energy								
Questions	(a)	(b)	(c)	Notes				
1			Х					
2		Х						
3	Х							
4		Х						
5		Х						
6			Х					
7			Х					
8.1		Х						
8.2			Х					
8.3	Х							

Second exercise: Role of a coil in a circuit

Questions	(a)	(b)	(c)	Notes
A.1			Х	
A.2	Х			
A.3			Х	
A.4			Х	
B.1.1		Х		
B.1.2	Х			
B.2		Х		
C.1		Х		
C.2	Х			
C.3			Х	