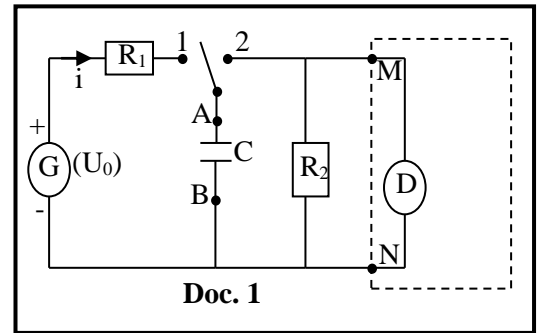


Simulation of the timing of a car's light

The circuit of the document (1) simulates the timing of the light a car .This circuit comprises:

- a generator delivering between its terminals a constant voltage $U_0 = 12\text{V}$;
- a capacitor initially uncharged and of capacitance $C = 470\mu\text{F}$
- two resistors R_1 and R_2 where R_1 and R_2 have respectively the resistances $R_1 = 100\Omega$ and $R_2 = 1000\Omega$;
- a small electronic circuit (D) which commands a lamp that remains lie as long as the potential difference u_{MN} is higher than 4.5V . We suppose that the circuit (D) does not influence the circuit of the capacitor .
- Connecting wires and a switch K which :
 - ✓ when the door of the car is opened , K passes in position (1) .
 - ✓ when the door is closed K passes in position (2) .



1-Charge of the capacitor

We open the door of the car at the instant $t_0 = 0$, that corresponds to putting the switch K on position (1) at $t_0 = 0$. At the instant t , the voltage across the capacitor is $u_c = u_{AB}$ and the circuit is traversed by a current i .

- 1.1) Using the law of addition of voltages , derive the differential equation describing the variation of the voltage u_c in terms of time .
- 1.2) The solution of this differential equation is of the form $u_c = A + B e^{-\frac{t}{\tau}}$ where A , B and τ are constants . Determine A , B and τ and specify the significance of τ .
- 1.3) Deduce the minimum duration at the end of which the capacitor will be supposed practically completely charged

2- Discharging the capacitor

We close the door of the car at an instant $t_0 = 0$, considering as new origin of time, which that corresponds to putting the switch K on position (2) at $t_0 = 0$.

- 2.1) Draw a figure of the new circuit showing the real direction of the discharging current i .
- 2.2) Show that the differential equation that governs the variations of u_c in terms of time is of the form :

$$\frac{du_c}{dt} + \frac{u_c}{R_2 C} = 0$$

2.3)

2.3.1) What is the initial value of u_c .

2.3.2) $u_c = D + F e^{-\alpha t}$ is a solution of this differential equation .

2.3.2.1) Determine the numerical values of the constants : D , F and α .

2.3.2.2) Draw the shape of the graph representing the variations of u_c in terms of time .


2.3.2.3) Show on the graph the point of abscissa $t = \frac{1}{\alpha}$.


2.4)

2.4.1) Deduce from the graph an approximate value of the duration , during which the lamp remains glowing after closing the door of car .

2.4.2) Determine this duration by calculation .

2.4.3) Will this duration be sufficient if we want that lamp shines between 5 and 10 seconds ?
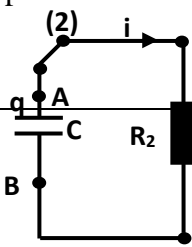
| P a r t | First exercise | P o i n t s |
|---------------------|---|----------------------------|
| 1. 1 | $+ \frac{1}{R_1 C} u_C = \frac{E}{R_1 C}.$ | 0. 5 |
| 2. 2 | <p>At $t_0 = 0$, $u_C = 0 \Rightarrow A + B = 0 ; \Rightarrow A = -B \Rightarrow u_C = A - A e^{-\frac{t}{\tau}}$</p> $\Rightarrow \frac{A}{\tau} e^{-\frac{t}{\tau}} - \frac{A}{R_1 C} e^{-\frac{t}{\tau}} + \frac{A}{R_1 C} = \frac{E}{R_1 C}$ $\Rightarrow A = E$ <p>and $\frac{1}{\tau} = \frac{1}{R_1 C} \Rightarrow \tau = R_1 C$</p> <p>$\tau$ time constant is the time needed for $u_C = 63\%$ of its maximum value E.</p> | 1 |
| 3. 3 | <p>Capacitor is totally charged $t = 5\tau = 5 \times 100 \times 470 \times 10^{-6} = 0.235$ s.</p>  | 0. 5 |
| 2. 1 | | 0. 5 |
| 2. 2 | $\frac{du_C}{dt}$ | 1 |
| 2. 3. 1 | At $t_0 = 0$, $u_C = E = 12$ V. | 0. 2 5 |
| 2. 3. 2. 1 | $\Rightarrow -\alpha F e^{-\alpha t} + \frac{1}{R_2 C} D + \frac{1}{R_2 C} F e^{-\alpha t} = 0$ $\Rightarrow D = 0;$ | 1. 5 |
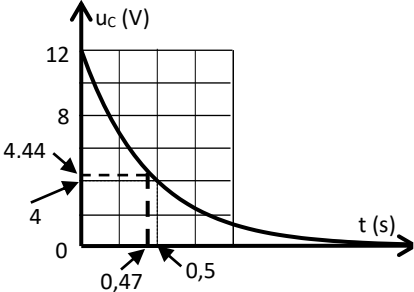
| | | | |
|---------------------|--|---|--------------|
| 2. 3. 2. 2 | $\frac{1}{\alpha} = 0.47 \text{ s}$ $u_C = 0.37 \times 12 = 4.44 \text{ V}.$ |  | 1 |
| 2. 4. 1 | At $u_{\min} = 4 \text{ V}$, $t = 0.5 \text{ s}$ | | 0. 2 5 |
| 2. 4. 2. 1 | $4 = 12 e^{-2.127t} \Rightarrow \ln(\frac{4}{12}) = -2.127 t = -1.098 \Rightarrow t = 0.52 \text{ s}.$ | | 0. 7 5 |
| 2. 4. 3 | Since 10 is greater than 2.35 s (5τ). | | 0. 2 5 |