

capacitors



Learning objectives

- Define a capacitor
- Define the capacitance of a capacitor.
- Give the expression of the capacitance of a parallel capacitor.
- Know the expression of the energy stored in a charged capacitor.
- Define the breakdown potential.
- Explain the charging and discharging of a capacitor (R-C series circuit, time constant $\tau = RC$)

Definition

- * A capacitor is an electric device formed of two conducting plates (called armatures) facing each other and separated by an insulator (dielectric).
- * when the armatures are plane and parallel then the capacitor is called parallel plane capacitor


1e

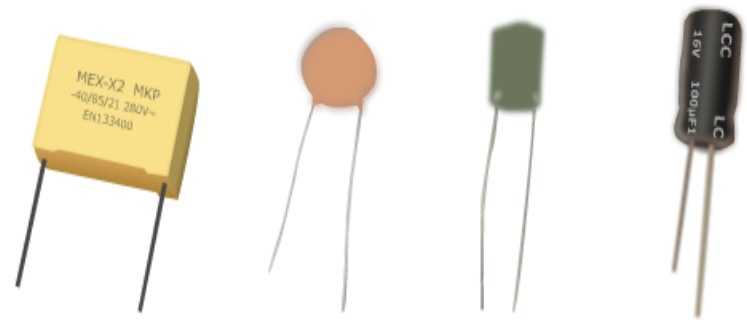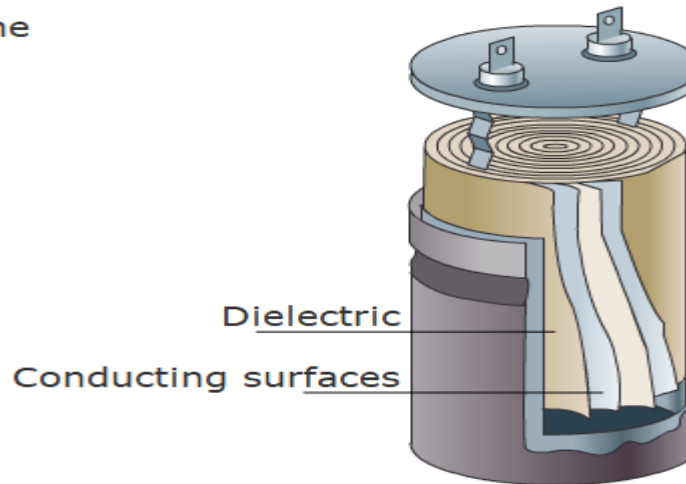




Charging of a capacitor

*If no excess or deficit of electrons on the plates of the capacitor, we say that the capacitor is neutral or uncharged.

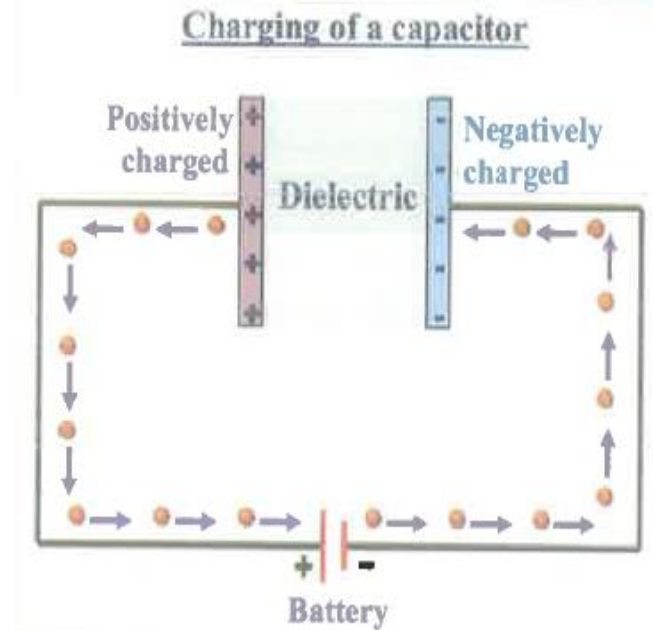*When a capacitor is connected across a battery, electrons flow from the negative pole of the battery to a plate of the capacitor connected to it. At the same rate, electrons flow from the other plate of the capacitor to the positive pole of the battery.



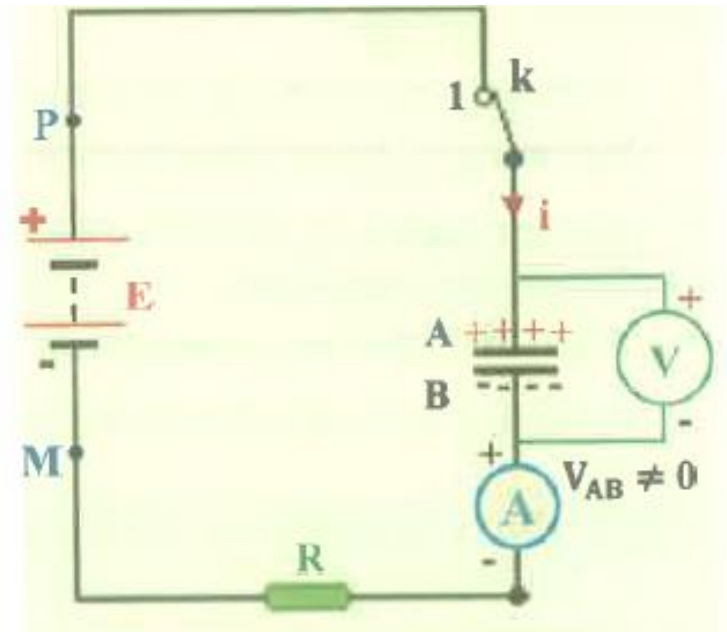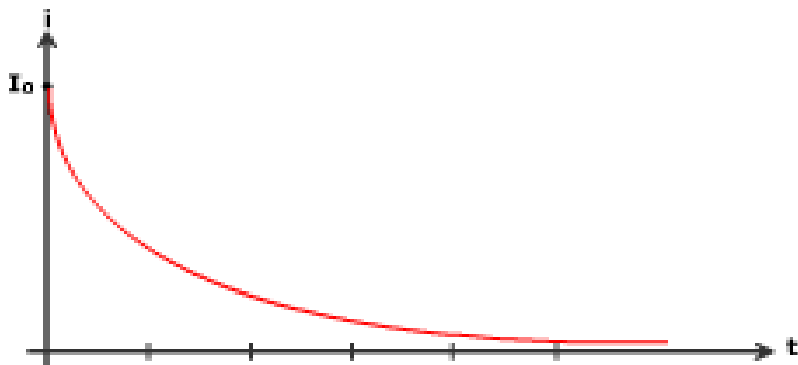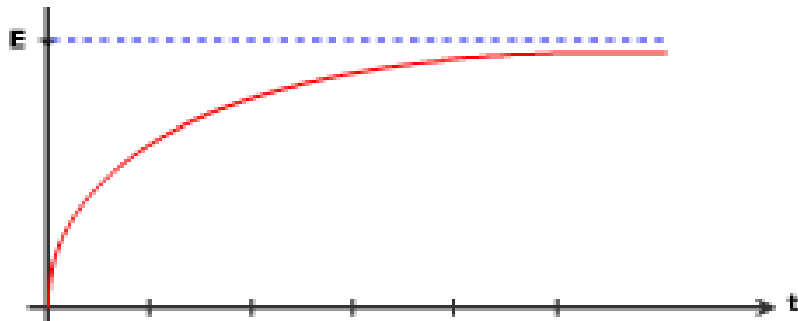- As charges accumulate on the plates of the capacitor, the potential difference across the plates increases while the current decreases .
- When $U_C = U_{PM} = E$ (e.m.f),
The current becomes zero and the capacitor is fully charged.
The charge of the capacitor $Q = q_A = -q_B = N e$
- **Note:** No current passing through the capacitor since there is a dielectric between the plates.



Capacitance of a capacitor

The charge of a capacitor is directly proportional to its voltage U where the ratio of proportionality between Q and U :

$Q/U = C = \text{constant} > 0$ it is called the **capacitance** of the capacitor that depends on the capacitor it self . Its unit in the SI units is the Farad (F)

Capacitance of a parallel plate capacitor

- * Dielectric is vacuum **or** air

$$\text{Capacitance } C_0 = \frac{Q}{V} = \epsilon_0 \frac{S}{d}$$

Where: S is the common area (m^2)


d distance between armatures (m)

ϵ_0 is the permittivity of the medium (air)

- * Dielectric is an insulating material : $C = \frac{Q}{V} = \epsilon \frac{S}{d}$

$\epsilon_r = \epsilon / \epsilon_0 > 1$ where ϵ_r is the relative permittivity of a dielectric and
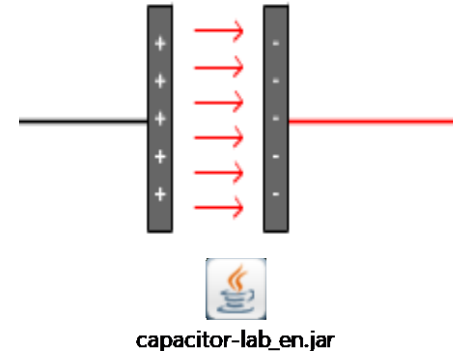
$$\epsilon_0 = \frac{1}{36\pi \times 10^9} = 8.85 \times 10^{-12} \frac{\text{C}}{\text{Nm}^2} \text{ or F/m}$$



Stored electric energy

Break down voltage:

Every dielectric has a limit of electric field E_{\max} whenever the field exceeds the maximum value it causes damage for the dielectric (becomes conductor)

$$E = \frac{U}{d} \rightarrow U_{\max} = d \times E_{\max} \text{ The break down potential}$$

Stored electric energy:

The electric energy stored in a capacitor is given as

$$W = \frac{1}{2} C U^2 = \frac{1}{2} Q U = \frac{1}{2} Q^2 / C$$

Note: During charging, the capacitor acts as a receiver (electric device)

Grouping capacitors

* **Definition:** the equivalent Capacitor is a single capacitor that replaces grouping of capacitors and acquires the same charge Q under the same voltage U .

Parallel connection:

$$Q_1 = C_1 U \text{ \& } Q_2 = C_2 U, Q = CU$$

$$\text{but } Q = Q_1 + Q_2$$

$$\rightarrow C_{eq} U = C_1 U + C_2 U$$

$$\rightarrow C_{eq} U = (C_1 + C_2) U$$



$$\text{Thus } C_{eq} = C_1 + C_2 + \dots C_n$$

Series connection: $Q_1 = Q_2 = Q$

$$U_1 = \frac{Q}{C_1} \text{ \& } U_2 = \frac{Q}{C_2} \text{ but } U = U_1 +$$

$$U_2 \text{ then } \frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$
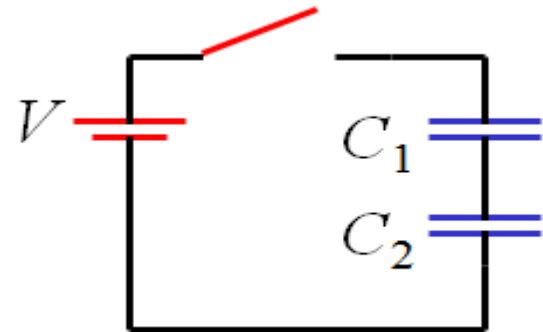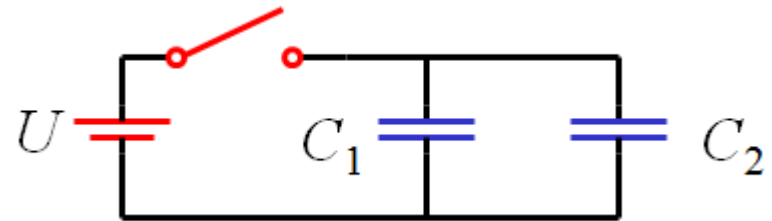
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots \frac{1}{C_n}$$



Time constant of R-C circuit

The time constant ($\tau = RC$) is the time taken by the capacitor to charge 63% of its maximum charge Q during charging phase.

Or




($\tau = RC$) It is the time taken by the capacitor to discharge 63% of its maximum charge Q during discharging phase.

Charging of a capacitor:

For $t_0 = 0$,
 $u_c = q_c = 0$
 $i_o = I_{\max} = E/R$

$t = \tau = RC$,
 $q = 0.63Q$,
 $u_c = 0.63U_{\max}$

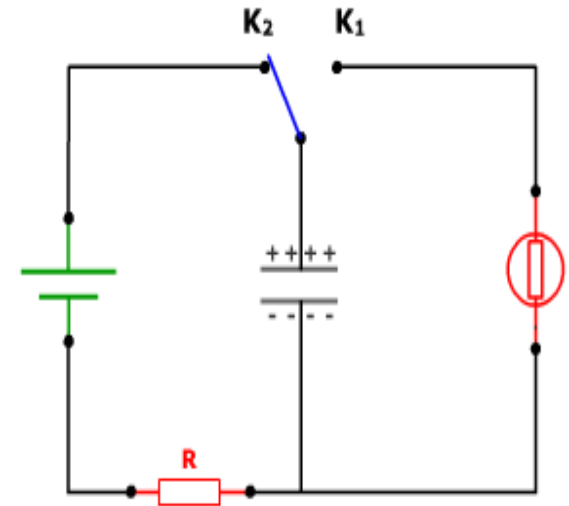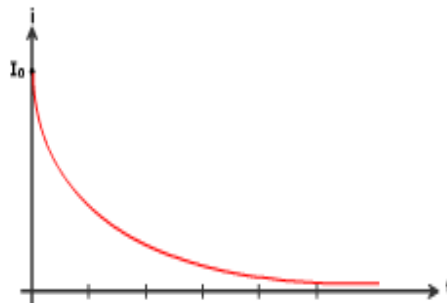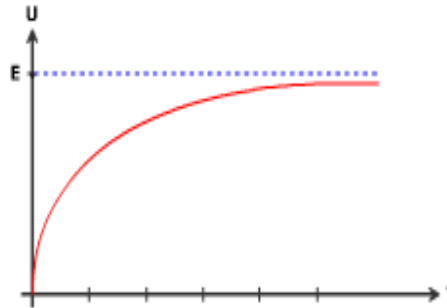$t \approx 5\tau = 5RC$,
 $u_c = U_{\max} = E$ (emf of G)
 $q = q_{\max} = Q$
 $i = 0$






Discharging of a capacitor

For $t_0 = 0$: $u_c = U_{\max} = E$ (emf of G), $q_c = q_{\max} = Q$, $i = -I_{\max} = -E/R$

$t = \tau = RC$: $q = 0.37Q$ $u_c = 0.37U_{\max}$

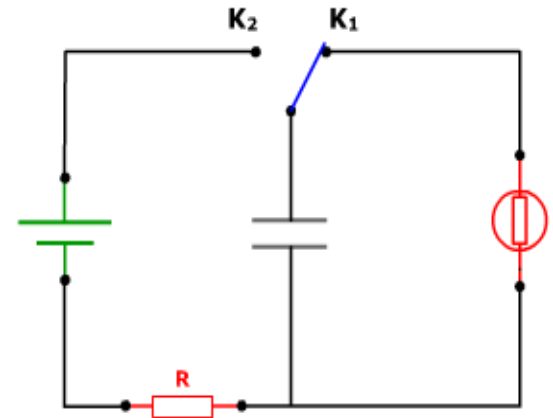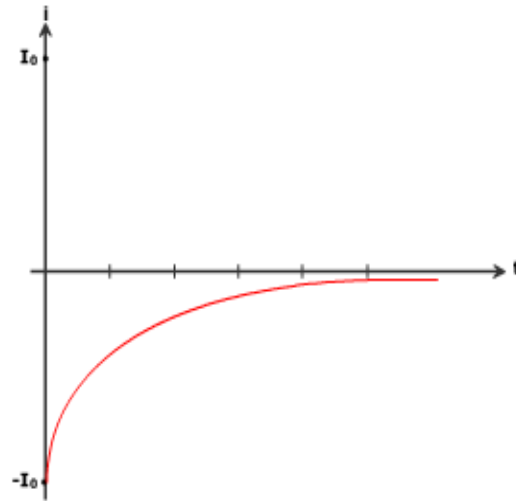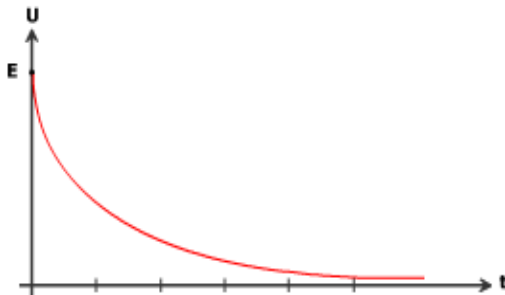$t \approx 5\tau = 5RC$: $q = u = 0$ $i = 0$



Animation from Phet And Edulab



capacitor-lab_en.jar

charging phase of the capacitor

1. Differential equation in voltage u_C

According to the law of addition of voltage

$$u_{AB} = u_{AM} + u_{MB}$$

$$u_G = u_R + u_C \quad \text{with: } u_C = u_{MB}, u_R = u_{AM}$$


$$E = Ri + u_C$$

$$\text{with } q = Cu_C \text{ and } i = + \frac{dq}{dt} = +C \frac{du_C}{dt}$$

$$\text{Then } E = RC \frac{du_C}{dt} + u_C$$

$$\text{or} \quad \frac{E}{RC} = \frac{du_C}{dt} + \frac{u_C}{RC}$$

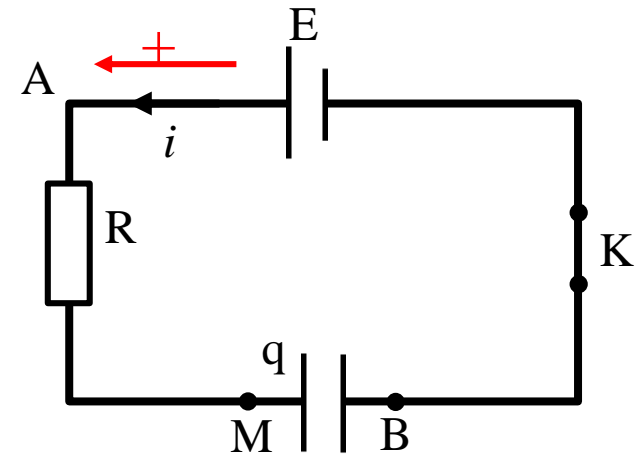This is first order differential equation that governs the variation of u_C with respect to time during charging phase



2. Solution of the differential equation

$$u_C = E(1 - e^{-\frac{t}{\tau}})$$

$$t = 0s:$$


$$u_C = E(1 - e^{-\frac{0}{\tau}}) = E(1 - 1) = 0V.$$

$$t = \tau:$$

$$u_C = E(1 - e^{-\frac{\tau}{\tau}}) = E(1 - 0.37) = 0.63 E$$

$$t = 5\tau:$$
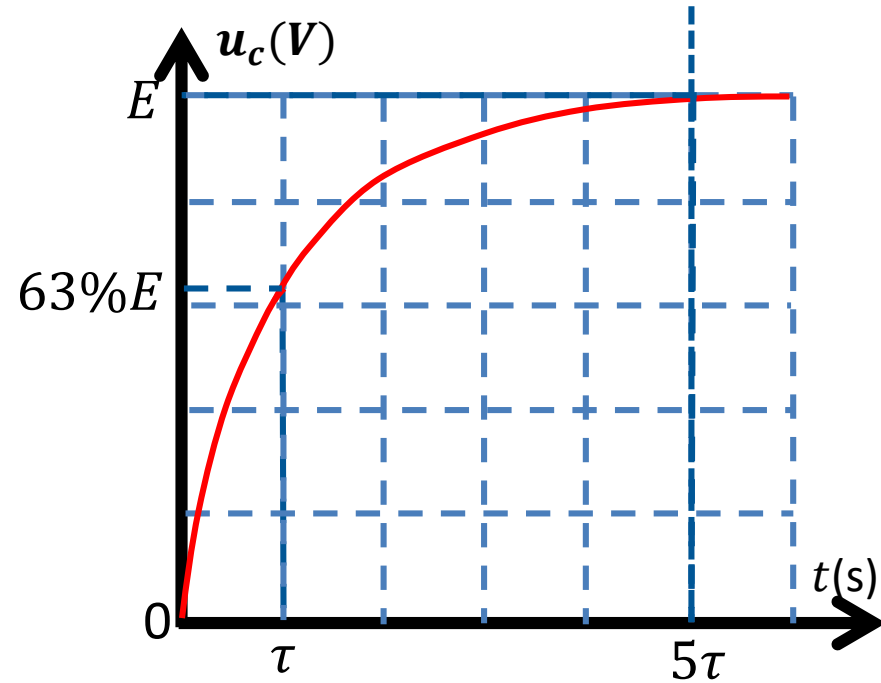
$$u_C = E(1 - e^{-\frac{5\tau}{\tau}}) = E(1 - 0.007) = 0.99 E$$



3. Verification of the solution :

$$u_C = E\left(1 - e^{-\frac{t}{\tau}}\right) \quad u_C = E - Ee^{-\frac{t}{\tau}}$$

$$\frac{du_C}{dt} = \frac{E}{\tau} e^{-\frac{t}{\tau}} \quad (e^u)' = u' e^u$$

Substitute in the differential equation: $\frac{E}{RC} = \frac{u_C}{RC} + \frac{du_C}{dt}$

$$\frac{E}{RC} = \frac{E(1 - e^{-\frac{t}{\tau}})}{RC} + \frac{E}{\tau} e^{-\frac{t}{\tau}}$$

$$\frac{E}{RC} = \frac{E}{RC} - \frac{E}{RC} e^{-\frac{t}{\tau}} + \frac{E}{RC} e^{-\frac{t}{\tau}}$$

$$\frac{E}{RC} = \frac{E}{RC} \text{ So the equation is verified}$$


4. Expression of the current i as function of time:

$$u_G = u_R + u_C \quad E = Ri + u_C$$

$$i = \frac{E - u_C}{R} = \frac{E - E\left(1 - e^{-\frac{t}{\tau}}\right)}{R}$$

$$= \frac{E - E + Ee^{-\frac{t}{\tau}}}{R} = \frac{+Ee^{-\frac{t}{\tau}}}{R}$$

$$i = I_m e^{-\frac{t}{\tau}}$$

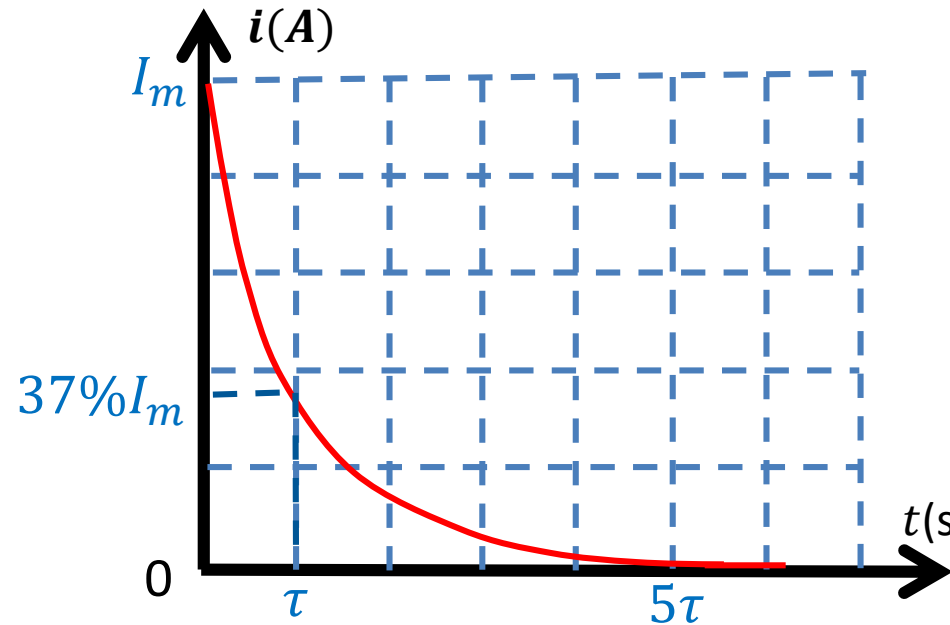

Or derive w.r.t time the eq. ($E = Ri + u_C$)

$$0 = R \frac{di}{dt} + \frac{du_c}{dt} = R \frac{di}{dt} + \frac{i}{C}$$

$$\frac{di}{dt} + \frac{i}{RC} = 0 \quad i = I_m e^{-\frac{t}{\tau}}$$

5. Calculation of the time constant τ :

Draw the tangent to the curve $u_C = f(t)$ at $t_0 = 0$.

Charging phase: $u_C = E(1 - e^{-\frac{t}{\tau}})$

$$\frac{du_C}{dt} = \frac{E}{\tau} e^{-\frac{t}{\tau}} \quad \left(\frac{du_C}{dt}\right)_{t=0} = \frac{E}{\tau}$$


From graph $\tan\theta = \frac{E}{t_1}$

by comparison, same slope $\frac{E}{t_1} = \frac{E}{\tau} \Rightarrow t_1 = \tau$

but $\frac{E}{RC} = \frac{du_C}{dt} + \frac{u_C}{RC}$
 $\left(\frac{du_C}{dt}\right)_{t=0} = \frac{E}{\tau}$ and $u_C = 0$ then $\frac{E}{RC} = \frac{E}{\tau}$, $\tau = RC$

Conclusion:

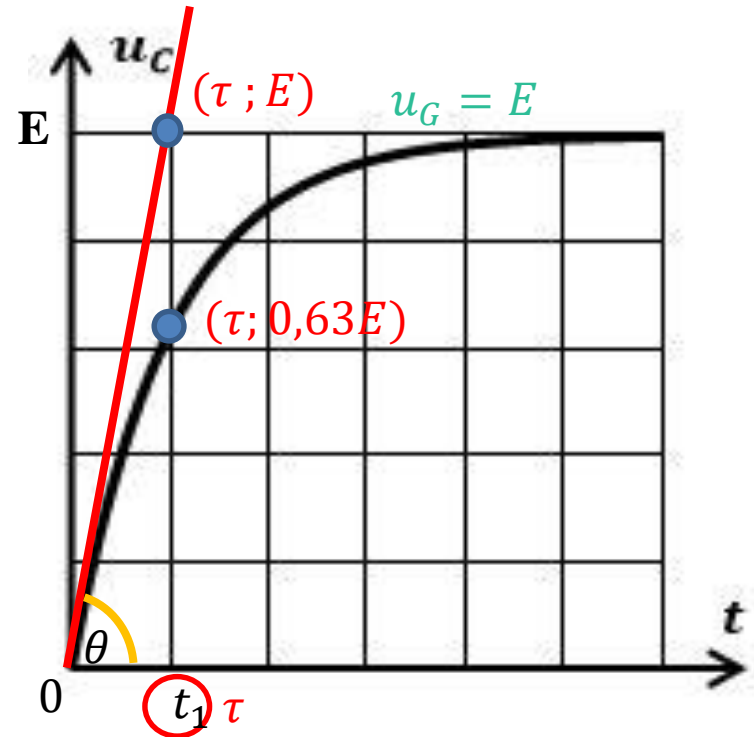The straight line tangent to the curve u_C at $t = 0$ cuts the horizontal asymptote $u = E$ at point of abscissa $t_1 = \tau = RC$



Discharging of a capacitor

1- Differential equation in voltage u_C

According to the law of addition of voltage

$$u_{MB} = u_{MA} + u_{AB}$$

$$u_{MB} = u_{MA} \quad (u_C = u_{MB} \quad ; \quad u_{MA} = Ri)$$

$$u_C = Ri$$


$$u_C - Ri = 0$$

$$u_C + RC \frac{du_C}{dt} = 0$$

$$\text{with } q = Cu_C \text{ and } i = -\frac{dq}{dt} = -C \frac{du_C}{dt}$$

$$\frac{du_C}{dt} + \frac{u_C}{RC} = 0$$

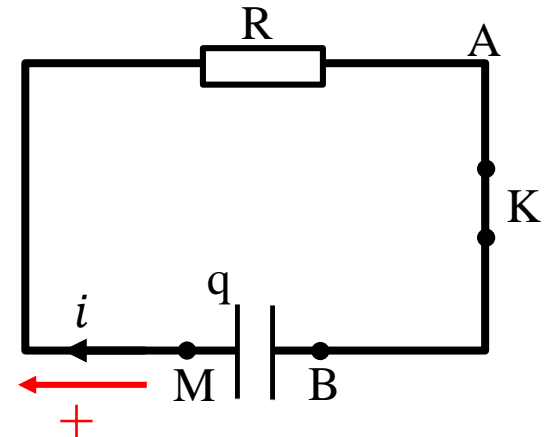First order differential equation that governs the variation of u_C with respect to time during discharging phase



2- Solution of the differential equation:

$$u_C = E e^{-\frac{t}{\tau}}$$

Where $\tau = RC$ is the time constant

For $t = 0$ s:


$$u_C = E(e^{-\frac{0}{\tau}}) = E(1) = E.$$

For $t = \tau$:

$$u_C = E(e^{-\frac{\tau}{\tau}}) = E(0,37) = 0,37E$$

For $t = 5\tau$:
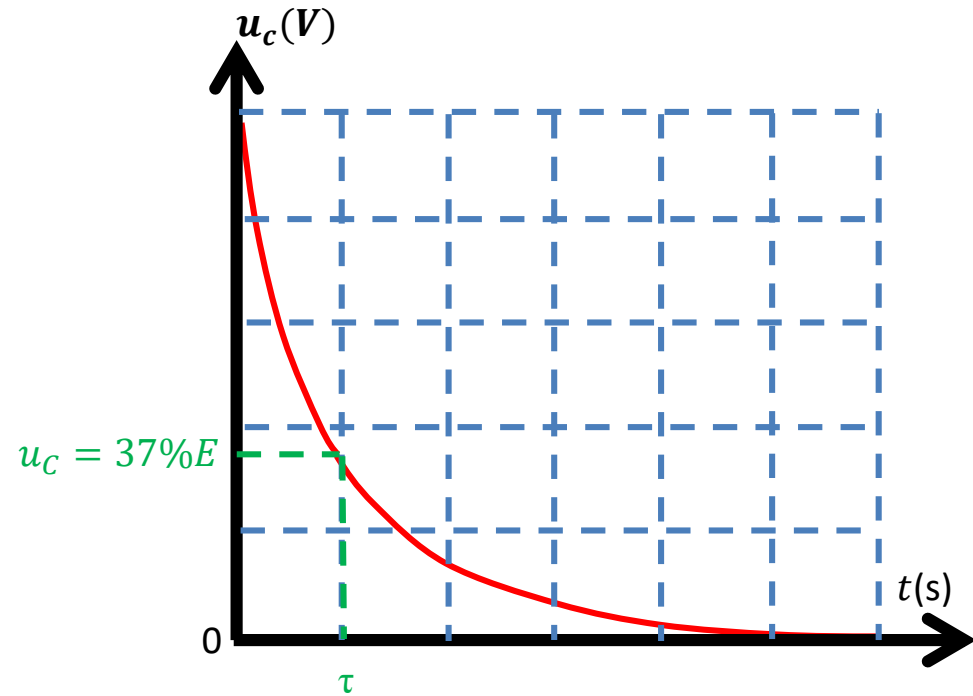
$$u_C = E(e^{-\frac{5\tau}{\tau}}) = E(0,007) = 0,007E$$



3- Verification of the solution :

$$u_C = E e^{-\frac{t}{\tau}}$$

Where $\tau = RC$

$$\frac{du_C}{dt} = -\frac{E}{\tau} e^{-\frac{t}{\tau}}$$


Substitute in the differential equation : $\frac{u_C}{RC} + \frac{du_C}{dt} = 0$

$$\frac{E e^{-\frac{t}{\tau}}}{RC} - \frac{E}{\tau} e^{-\frac{t}{\tau}} = 0$$

$$\frac{E e^{-\frac{t}{\tau}}}{RC} - \frac{E}{RC} e^{-\frac{t}{\tau}} = 0$$

$$0 = 0$$

So the solution is verified

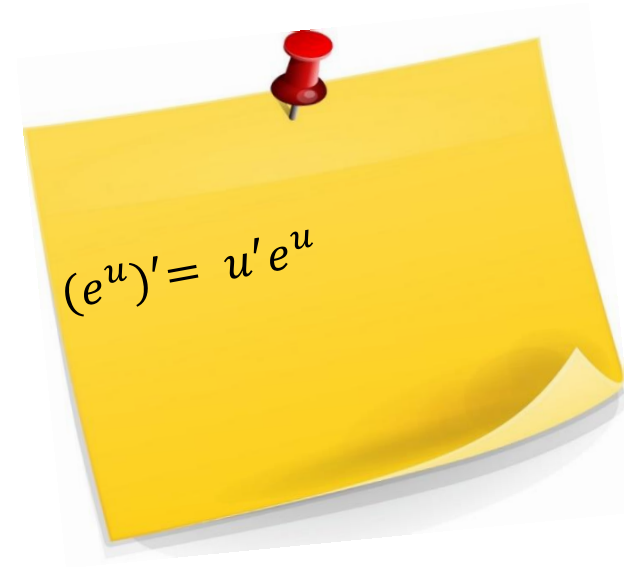

4- Finding the time constant τ

The tangent to the curve $u_c = f(t)$ at $t_0 = 0$

$$u_c = E e^{-\frac{t}{\tau}}$$

$$\frac{du_c}{dt} = -\frac{E}{\tau} e^{-\frac{t}{\tau}} \quad \left(\frac{du_c}{dt}\right)_{t=0} = -\frac{E}{\tau}$$

Slope of the straight line: $\frac{\Delta u}{\Delta t} = \frac{0-E}{t_1-0} = -\frac{E}{t_1}$

by comparison: $-\frac{E}{t_1} = -\frac{E}{\tau} \Rightarrow t_1 = \tau$


Use diff. Equation $\frac{du_c}{dt} + \frac{u_c}{RC} = 0$

$$t = 0s, \quad \frac{du_c}{dt} + \frac{E}{RC} = 0 \quad \frac{du_c}{dt} = \frac{-E}{RC} = -\frac{E}{\tau} \quad \tau = RC$$

Conclusion:

The straight line tangent to the curve u_c at $t = 0$ cuts the horizontal asymptote $u = E$ at point of abscissa

$$t_1 = \tau = RC$$

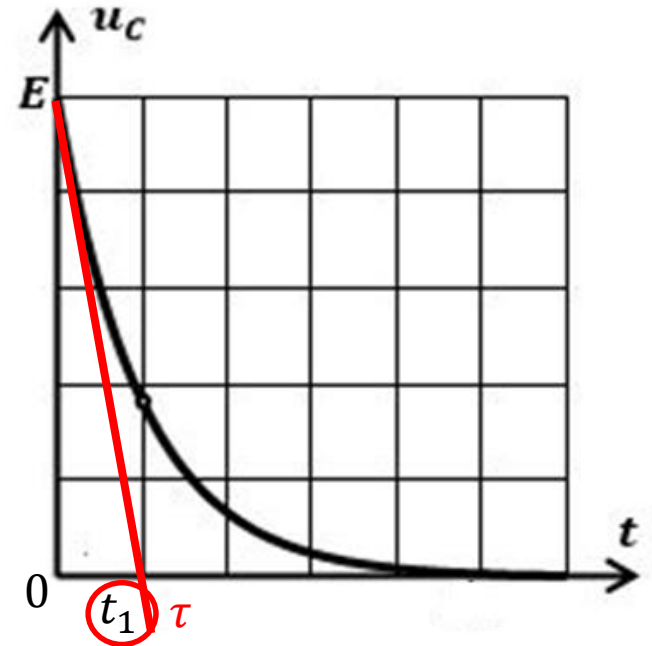

5- Expression of the electric current i during time :

$$u_{MB} = u_{MA} \quad u_C = Ri$$

$$i = \frac{u_C}{R} = \frac{E e^{-\frac{t}{\tau}}}{R} \quad i = I_m e^{-\frac{t}{\tau}}$$

Or derive wrt time:

$$\frac{du_C}{dt} = R \frac{di}{dt}$$

$$\text{But } i = -\frac{dq}{dt} = -C \frac{du_C}{dt} \quad \frac{du_C}{dt} = \frac{-i}{C}$$

$$\frac{di}{dt} + \frac{i}{RC} = 0 \quad i = I_m e^{-\frac{t}{\tau}}$$

