

Principle of neon tube using a capacitor

A neon discharging tube is an electric dipole that lights up if the voltage across its terminals is greater than a specific voltage U_a and puts off when the voltage across its terminals becomes less than a certain voltage U_e ($U_e < U_a$) called cut off voltage.

This lamp behaves as an open switch when it is off and as a resistor of resistance R' when it is on.

To study the functioning of this dipole we consider the following circuit (Doc.1) **K** is an automatic switch that connects and disconnect the generator at specific time intervals.

1- The tube is turned off . ($R = 100 \text{ k}\Omega$; $C = 10 \text{ }\mu\text{F}$).

1.1-What is the phenomenon observed across the terminals of the capacitor ?

1.2- Establish the differential equation describing the variations of the voltage $u_C = u_{MN}$ across the terminals of the capacitor.

1.3-The solution of the differential equation is $u_C = A(1 - e^{-\frac{t}{\tau}})$.

1.3.1-Determine the expressions of the constants A and τ .

1.3.2- Name the constant τ , give its significance and calculate its value.

1.4-

1.4.1- Verify that if the tube is not connected to the circuit, the maximum voltage u_C can attain is E

1.4.2- Indicate the time interval during which the maximum voltage is attained practically

1.4.3-The document (2) represents u_C as a function of time during charging and discharging the capacitor. Determine the value of E graphically.

2- The tube is turned on

2.1-Determine, graphically the value U_a at which the tube is on.

2.2-Determine , graphically the voltage U_e



2.3- Deduce the duration of lightening of the tube.

2.4- Calculate the average power received by the tube during this lighting phase.

2.5- Let $u_C = U_a e^{-\frac{t}{\tau}}$ the voltage across the terminals of the capacitor during its discharging starting from the instant $t=0$ taken as origin of time .

2.5.1-Calculate the value of τ .

2.5.2-Deduce the value of R' .

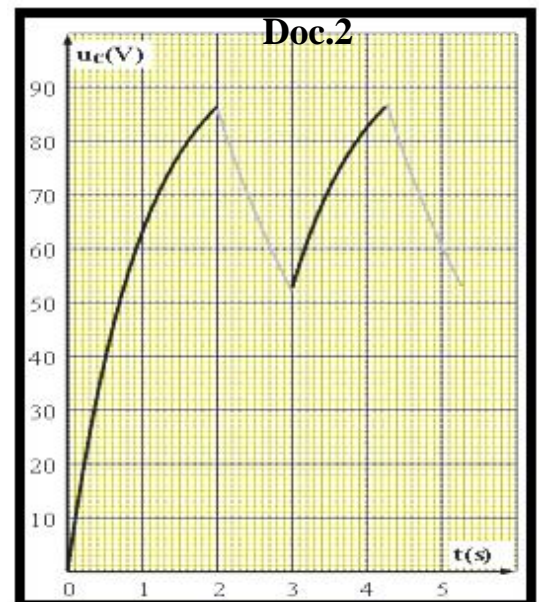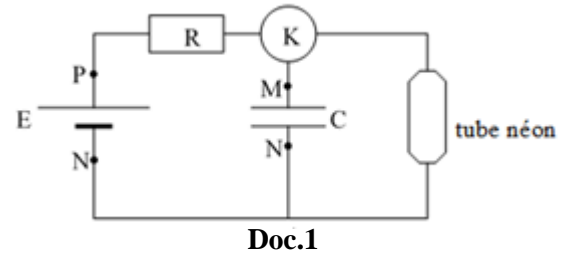

Part		Principle of neon tube using a capacitor	Score 6.5
1	1.1.	Charging of capacitor	0.25
	1.2	law of addition of voltages $\Rightarrow E = u_R + u_C$ leads to $\frac{du_C}{dt} + \left(\frac{1}{RC}\right)u_C = \frac{E}{RC}$	0.75
	1.3.1	$\frac{du_C}{dt} = \frac{A}{\tau} e^{-\frac{t}{\tau}} \Rightarrow \frac{A}{\tau} e^{-\frac{t}{\tau}} + \frac{1}{RC} A \left(1 - e^{-\frac{t}{\tau}}\right) - \frac{E}{RC} = 0$ $A e^{-\frac{t}{\tau}} \left(\frac{1}{\tau} - \frac{1}{RC}\right) + \frac{1}{RC} (A - E) = 0 \Rightarrow \begin{cases} \tau = RC \\ A = E \end{cases}$	0.75
	1.3.2	τ : is the time constant of RC circuit . duration of a neutral capacitor during charging for u_C to attain $0.63E$ $\tau = 1s$	0.5
	1.4.1	if the tube is not connected to the circuit , the steady state attained ($i=0$ and $u_R=0 \Rightarrow u_{C(max)} = E$).	0.25
	1.4.2	The state is practically attained after 5τ ($t > 5\tau$)	0.25
	1.4.3.	from (Doc.2) $0.63 E = 63 V \Rightarrow E = 100V$	0.5
2	2.1	(Doc.2) functioning of the tube at $t = 2s \Rightarrow U_a = 85V$	0.25
	2.2	(Doc.2) cut of voltage at $t=3s$ during its discharge $U_e=54V$,	0.5
	2.3	The tube lights for $\Delta t = 1s$ during which the capacitor is discharged in the tube of resistance R'	0.5
	2.4	$E_e = \frac{1}{2} C u^2$ $P_{av} = \frac{\Delta E_e}{\Delta t} = \frac{C}{2\Delta t} \left[(U_e)^2 - (U_a)^2 \right]$ $P_a = -2.15 \times 10^{-2} J$	1
	2.5.1	$U_e = U_a e^{-\frac{1}{R'C}} \Rightarrow \frac{U_e}{U_a} = e^{-\frac{1}{\tau'}} \Rightarrow \frac{1}{\tau'} = \ln\left(\frac{U_a}{U_e}\right)$ $\tau' = \frac{1}{\ln\left(\frac{U_a}{U_e}\right)} = 2.2s$	1
	2.5.2	$R' = \tau'/C = 2.2 \times 10^5 \Omega$	0.5