

Capacitor

. Recall

$$i = \frac{dq}{dt}$$

$$U_C = \frac{q}{C}$$

$$\rightarrow q = C \cdot U_C$$

$$\text{then } i = \frac{d[C \cdot U_C]}{dt} = C \frac{dU_C}{dt} = i$$

→ Charging of Capacitor

applying law of addition of voltages:

$$E = U_C + U_R$$

$$\text{at } t=0 : U_C = 0 \rightarrow E = R \cdot I.$$

$$\rightarrow I = \frac{E}{R}$$

$$U_C = \frac{q}{C} = \int \frac{i}{C} dt$$

$t \neq 0$: $U_C \uparrow$ and $U_R \downarrow$

$$\text{then } E = U_C + U_R$$

$$t = \infty \Rightarrow U_R = 0$$

$$\downarrow \rightarrow E = U_C$$

($U_R = R \cdot i = 0$
then $i = 0$)

$$\text{steady phase: } Q = CE = Cst \rightarrow \frac{dq}{dt} = 0 \rightarrow i = 0 \quad (i = \frac{dq}{dt})$$

Note: $i = 0$ then resistor acts as connecting wire.

→ D.E of charging

* in V_C :

law of addition of voltages

$$E = V_C + V_R$$

$$E = V_C + R_i$$

$$\therefore RL \left(E = V_C + RC \frac{dV_C}{dt} \right)$$

$$\text{where } i = \frac{C dV_C}{dt}$$

$$\frac{dV_C}{dt} + \frac{V_C}{RC} = \frac{E}{RC}$$

* in q :

law of addition...

$$E = V_C + R_i$$

$$\therefore R \left(E = \frac{q}{C} + R \frac{dq}{dt} \right)$$

$$\text{where } i = \frac{dq}{dt} \text{ and } V_C = \frac{q}{C}$$

$$\rightarrow \frac{dq}{dt} + \frac{q}{RC} = \frac{E}{R}$$

→ Solution of D.E

$$V_C = E(1 - e^{-t/\tau}) \quad \text{or} \quad q = Q_{\max}(1 - e^{-t/\tau})$$

given

$$\tau = RC$$

$$Q_{\max} = CE$$

. we substitute the solution in the D.F

* to get formula of current i :

$$V_C = E(1 - e^{-t/\tau})$$




$$i = C \frac{dV_C}{dt} \rightarrow i = C \frac{d}{dt} [E(1 - e^{-t/\tau})]$$

$$= CE \left[0 + \frac{1}{RC} e^{-t/\tau} \right]$$

$$= \frac{CE}{RC} e^{-t/\tau} = \frac{E}{R} e^{-t/\tau} = \boxed{\frac{I}{R} e^{-t/\tau}} = i$$

[Same for
 $q = C [E(1 - e^{-t/\tau})]$]

→ Shapes of charging

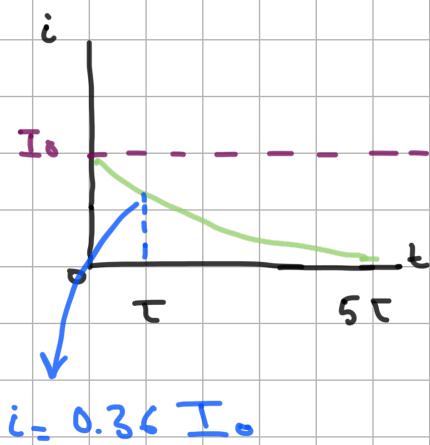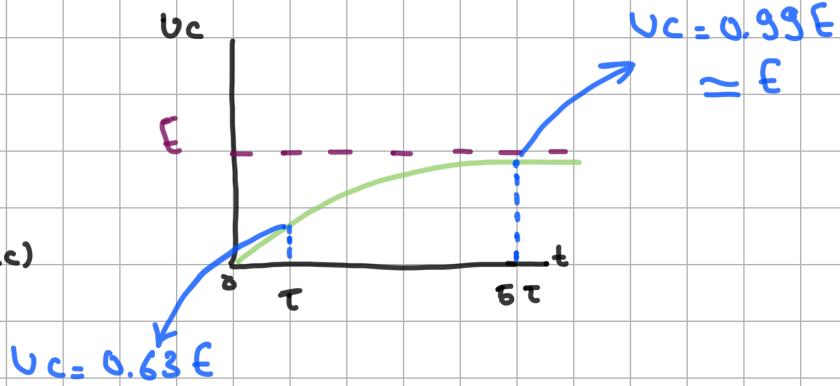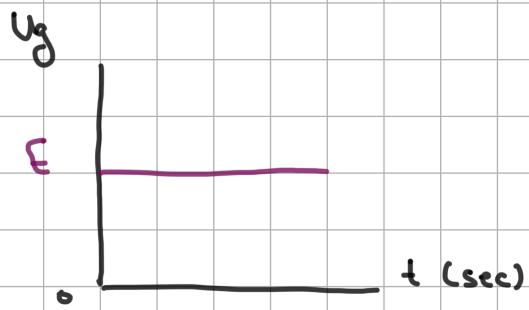

→ Discharging of Capacitor

now capacitor acts as generator
 (yani i bvtl3 mn i positive armature of $C \rightarrow 3ks$
 legeh li ega fi bl charging)

Law of addition of voltages

$$E = U_C + U_R$$

$$0 = U_C + R_i$$

$$t=0 : U_C = E \quad U_R = 0$$

$$t \neq 0 : U_C \downarrow \text{ and } U_R \uparrow$$

$$t \rightarrow \infty : U_C = 0 \quad U_R = E$$

→ D.F of Discharging

* in U_C :

Law of ...

$$0 = U_C + R_i$$

$$(0 = U_C + RC \frac{dU_C}{dt}) \div RC$$

$$\frac{dU_C}{dt} + \frac{U_C}{RC} = 0$$

* in q :

$$0 = U_C + R_i \\ \therefore R(0 = \frac{q}{C} + R \frac{dq}{dt})$$

$$\frac{dq}{dt} + \frac{q}{RC} = 0$$

→ Solutions

$$U_C = E e^{-t/RC}$$

$$\rightarrow i = C \frac{dU_C}{dt}$$



$$= C \frac{d}{dt} [E e^{-t/RC}]$$

$$= CE \times \frac{-1}{RC} e^{-t/RC}$$



$$= -\frac{C}{R} e^{-t/RC}$$

$$= -I_0 e^{-t/RC}$$

→ Shapes of Discharging

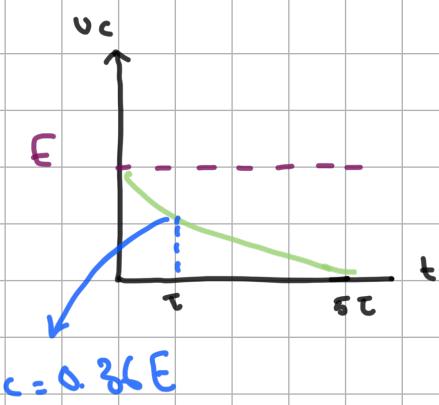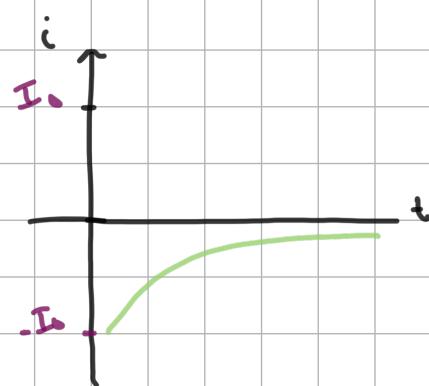

Note: bhar charging + discharging

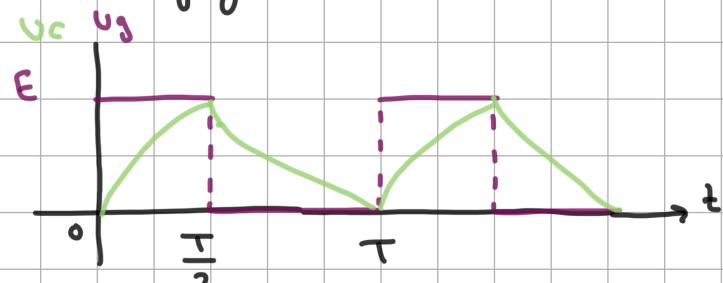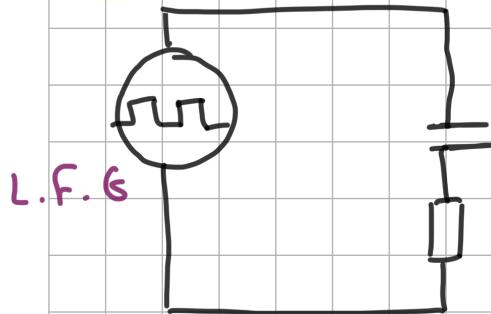

→ Energy in Capacitor

$$W = \frac{1}{2} QU \quad \text{or} \quad \frac{1}{2} CU^2 \quad \text{or} \quad \frac{Q^2}{2C}$$