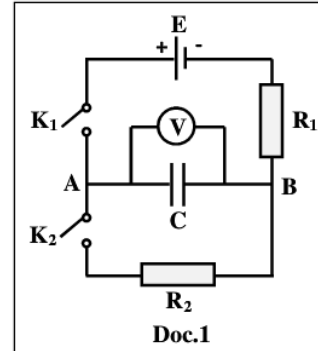


## Extra sheet (Capacitor)

### Exercise 1:

In order to determine the capacitance  $C$  of a capacitor, we connect up the circuit of document 1. This circuit is formed of the capacitor, a generator of e.m.f.  $E = 9V$  and of negligible internal resistance, two resistors of resistances  $R_1 = 200k\Omega$  and  $R_2 = 100k\Omega$  and two switches  $K_1$  and  $K_2$ .



#### I- Charging the capacitor


The capacitor being initially uncharged, we close  $K_1$  and keep  $K_2$  open. The capacitor will be charged.

- 1- Derive the differential equation that describes the variation of the voltage  $u_C = u_{AB}$  across the capacitor.
- 2- Knowing that the solution of this differential equation has the form  $u_C = E \left(1 - e^{-\frac{t}{\tau_1}}\right)$ . Determine the expression of the constant  $\tau_1$  as a function of  $R_1$  and  $C$ .
- 3- At the instant  $t_1 = 20s$ ,  $u_C$  has a value of  $7.78V$ . Calculate the capacitance  $C$  of the capacitor.
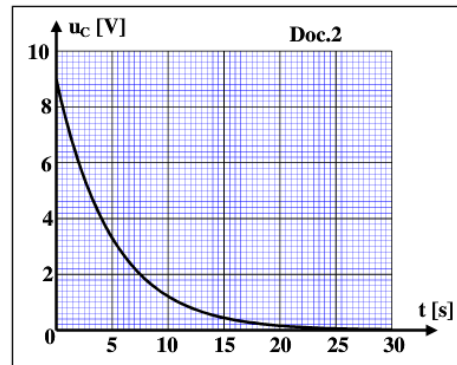
#### II- Discharging the capacitor

The capacitor being charged under a voltage of  $9V$ , we open  $K_1$  and close  $K_2$ . The capacitor then discharges.

- 1- Draw a diagram of the circuit during that phase indicating the direction of the current.
- 2- Derive the differential equation that describes the variation of the voltages  $u_C = u_{AB}$  across the capacitor.
- 3- Knowing that the solution of this differential equation is of the form  $u_C = E e^{-\frac{t}{\tau_2}}$ , deduce the expression of:
  - 3.1- the current  $i$  as a function of time. Take the direction of the current as a positive direction.
  - 3.2- the time constant  $\tau_2$  as a function of  $R_2$  and  $C$ .
- 4- A convenient apparatus allows us to trace the graph of the variation of  $u_C$  as a function of time. (document 2)  
Determine from the curve the value of  $\tau_2$ .  
Deduce the value of  $C$ .




#### III- What conclusion can be drawn about the two values of $C$ ? Comment.

### Exercise 2:

The object of this exercise is to distinguish the response of an RC series circuit when we apply across its terminals a constant voltage, from its response when it carries a constant current.
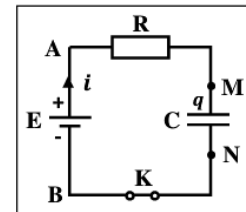
#### A- Case of a constant voltage

The circuit of the adjacent figure allows us to charge the capacitor of capacitance  $C = 10\mu F$  through a resistor of resistance  $R = 100k\Omega$ , under a constant voltage  $E = 9V$ . Take the instant  $t = 0$  the instant when the switch  $K$  is closed.




- 1- Denote by  $u_C = u_{MN}$ , the instantaneous value of the voltage across the terminals of the capacitor.
  - 1.1- Show that the differential equation in  $u_C$  is of the form:  $u_C + RC \frac{du_C}{dt} = E$ .
  - 1.2- Knowing that the solution of this equation has the form:  $u_C = A \left(1 - e^{-\frac{t}{\tau}}\right)$  determine  $A$  and  $\tau$ .
  - 1.3- Trace the shape of the curve that gives the variation of  $u_C$  as a function of time.
- 2-
  - 2.1- Determine the expression of the voltage  $u_R = u_{AM}$  as a function of time.

2.2- Trace, on the same system of axes, the shape of the curve giving the variation of  $u_R$  as a function of time.

3- What is the value of the interval if time  $t_A$  at the end of which  $u_C$  becomes practically 9V?
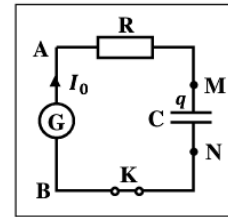
#### B- Case of a constant current

The preceding capacitor being discharged is to be recharged through the same resistor by a generator giving a constant current  $I_0 = 0.1\text{mA}$ .



1-

1.1- Show that the charge  $q$  can be written, in SI, in the form  $q = 10^{-4} \times t$ .

1.2- The voltage  $u_R = u_{AM}$  across the resistor remains constant. Determine its value.

1.3- Trace the shape of the graph representing  $u_R$ .

2-

2.1- Determine the expression of the voltage  $u_C = u_{MN}$  as a function of time.

2.2- Trace the shape of the graph representing  $u_C$ .

2.3- Determine the time interval  $t_B$  needed for the voltage  $u_C$  to attain the value 9V.

#### C- Conclusions


1- Using the preceding graphs, specify the case where the voltage across the capacitor attains, in the steady state, a limiting value.

2- A camera is equipped with a flash that is formed of the preceding RC circuit. We intend to take the largest number of photos in a given time interval. To do so we have to charge the capacitor. Which one of the two preceding charging modes is more convenient? Why?
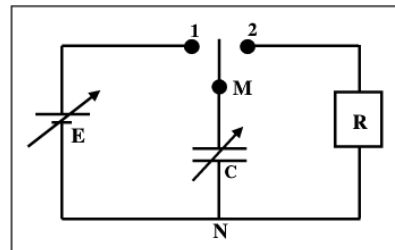
#### Exercise 3:

A heart suffering from disordered muscular contractions is treated by applying electric shocks using a convenient apparatus.

In order to study the functioning of this apparatus, we use a source of DC voltage of adjustable value  $E$ , a double switch, a resistor of resistance  $R$  and a capacitor (initially neutral) of adjustable capacitance  $C$ . We connect the circuit represented in the adjacent figure.



#### A. Theoretical study

1- The switch is turned to position (1).

1.1- Give the name of the physical phenomenon that takes place in the capacitor.

1.2- Specify the values of the current in the circuit and the voltage  $u_{MN}$  after few seconds.

2- The switch is now turned to position (2) at an instant taken as  $t_0 = 0$ .

2.1- Derive, at the instant  $t$ , the differential equation giving the variation of the voltage  $u_C = u_{MN}$  as a function of time.

2- The discharging starts at the instant  $t_0 = 0$ . At the instant  $t_1$ , the energy delivered to the patient amounts to 360J, the switch is then opened.

2.1- Calculate the energy that remains in the capacitor at the instant  $t_1$ .

2.2- Using the results of the above theoretical study; determine:

2.2.1- the value of  $t_1$ .

2.2.2- the current at the end of the electric shock.

**Exercise 4:**

The object of this exercise is to determine the capacitance of a capacitor and study the effect of certain physical quantities on the duration of its charging.

The circuit of figure (1) is formed of:

- an ideal generator delivering across its terminals an adjustable DC voltage  $u_{MN} = u_g = E$ ;
- a resistor of adjustable resistance  $R$  ;
- a capacitor of capacitance  $C$  ;
- a switch  $K$ .

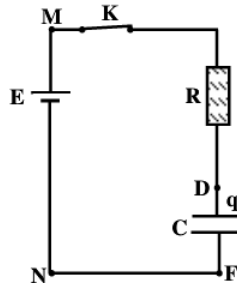


Figure 1

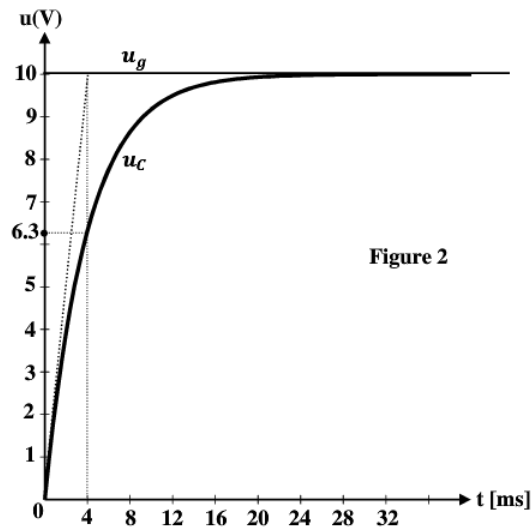


Figure 2

**I-** The value of  $E$  is adjusted at  $E = 10V$  and that of  $R$  at  $R = 2k\Omega$ .

The capacitor being initially neutral, we close the switch at the instant  $t_0 = 0$ .

**1-**

**1.1-** Derive the differential equation giving the variation of the voltage  $u_{DF} = u_C$  across the capacitor as a function of time.

**1.2-** Verify that the solution of this differential equation is  $u_C = E \left( 1 - e^{-\frac{t}{RC}} \right)$ .

**2-** The voltages  $u_C$  and  $u_g$  are displayed using an oscilloscope (figure 2).

**2.1-** Redraw the circuit of figure (1) showing the connections of the oscilloscope.

**2.2-** Give the maximum value of  $u_C$ .

**3-** One method to determine the value of  $C$  consists of determining the duration  $t_1$  at the end of which the voltage  $u_C$  attains 63% of its maximum value.

**3.1-** Show that  $t_1$  is very close to the value of  $RC$ .

**3.2-** Using figure (2), determine the value of the capacitance  $C$ .

**4-** Another method allows us to determine  $C$  starting from the tangent at  $O$  to the curve  $u_C = f(t)$  (fig.2).

**4.1-** Find the expression of  $\frac{du_C}{dt}$ , at  $O$ , in terms of  $E$ ,  $R$  and  $C$ .

**4.2-** Show that the equation of this tangent to the curve is  $u = \frac{E}{RC} t$ .

**4.3-** Verify that this tangent intersects the asymptote to the curve at the point of abscissa  $t_1 = RC$ .

**4.4-** Determine then the value of the capacitance  $C$  of the capacitor.

**II-** The value of  $R$  is adjusted at  $R = 1k\Omega$ .

**1-** Trace , on the same system of axes, the shape of the curve  $u_C$  in the two following cases :

Case (1):  $E = 10V$ ,  $C = 2 \times 10^{-6} F$  (curve 1)

Case (2):  $E = 5V$ ,  $C = 2 \times 10^{-6} F$  (curve 2)

Scale: on the axis of abscissas: 1 div  $\leftrightarrow$  4 ms; on the axis of ordinates: 1 div  $\leftrightarrow$  1 V.


**2-** Specify, with justification, which of the two physical quantities  $E$  or  $R$  affects the duration of charging of the capacitor.

### Exercise 5:

An electric component (D), of unknown nature, which may be a resistor of resistance  $R$  or a pure coil of inductance  $L$  or a capacitor of capacitance  $C$ . To determine the nature and the characteristic of (D) we consider the following:

- An ideal generator  $G$  of constant electromotive force (e.m.f)  $E$ ;
- Two resistors of resistances  $R_1 = 100\Omega$  and  $R_2 = 150\Omega$ ;
- A double switch  $K$ .


We set up the circuit of figure 1.

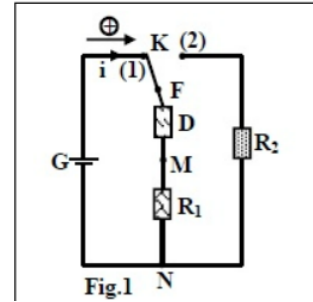
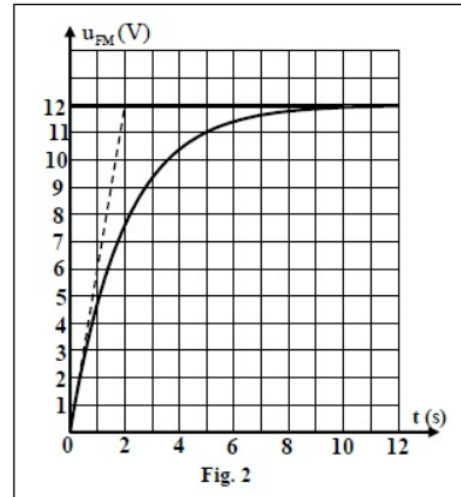
#### A- First Experiment

At an instant  $t_0 = 0$ , the switch  $K$  is turned to position (1). Figure 2 shows the variation of the voltage  $u_{FM}$  across the terminals of (D) as a function of time and the tangent to this curve at  $t_0 = 0$ .


- 1- The component (D) is a capacitor. Justify.
- 2- Indicate the value of the e.m.f  $E$  of the generator.
- 3- Calculate, at  $t_0 = 0$ , the current carried by the circuit.
- 4- Derive the differential equation describing the variation of the voltage  $u_{FM} = u_C$ .
- 5- The solution of the differential equation has the form:  
$$u_C = u_{FM} = A + Be^{-\frac{t}{\tau}}.$$
Determine the expressions of the constants  $A$ ,  $B$  and  $\tau$  in terms of  $R_1$ ,  $C$  and  $E$ .
- 6- Determine, graphically, the value of the time constant.
- 7- Deduce the value of  $C$ .



#### B- Second Experiment

During the charging of the capacitor and at an instant  $t_1$ , we turn the switch  $K$  to the position (2) (figure 3).

- 1- Name the phenomenon that takes place.
- 2- The resistor  $R_2$  can support a maximum power of  $P_{max} = 0.24W$ .
  - 2.1- Calculate the maximum value of the current which can pass through  $R_2$  without damaging it (the thermal power is given by the relation:  $p = Ri^2$ ).
  - 2.2- Applying the law of addition of voltages, show that the maximum voltage across the terminals of the capacitor is  $u_{FM} = 10V$  so that  $R_2$  will not be damaged.
  - 2.3- At the instant  $t_1$  the current is maximum. Determine, graphically, the maximum duration  $t = t_1$  of the charging process of the capacitor so that the resistor  $R_2$  will not be damaged.

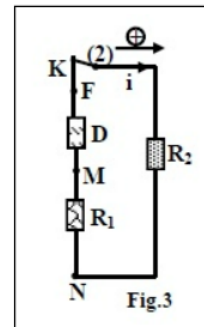

**Exercise 6:**



We intend to determine the resistance  $R$  of a resistor ( $R$ ). We thus connect up the circuit represented in figure (1) that is formed of an ideal generator of e.m.f  $E = 5\text{V}$ , the resistor ( $R$ ), an uncharged capacitor ( $C$ ) of capacitance  $C = 33\mu\text{F}$  and a double switch ( $K$ ).

**A- Charging of the capacitor**

- 1- We intend to charge the capacitor. To what position, 1 or 2, must then ( $K$ ) be moved?
- 2- The circuit reaches a steady state after a certain time. Give then the value of the voltage  $u_{AB}$  across ( $C$ ) and that of the voltage across ( $R$ ).

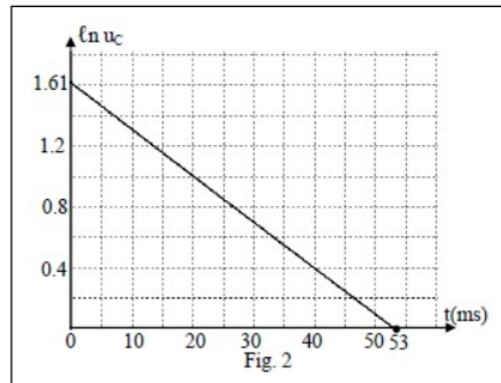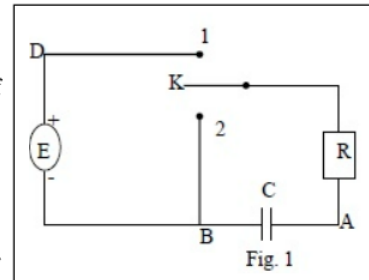**B- Discharging of the capacitor**

- 1- Draw a diagram of the circuit during the discharging of the capacitor and show on it the direction of the current it carries.
- 2- Derive the differential equation in  $u_C = u_{AB}$  during the discharging.
- 3- The solution of this differential equation has the form:  
 $u_C = E e^{-\frac{t}{\tau}}$  ( $u_C$  in V,  $t$  in s) where  $\tau$  is a constant.
  - 3.1- Determine the expression of  $\tau$  in terms of  $R$  and  $C$ .
  - 3.2- Determine the value of  $u_C$  at the instant  $t_1 = \tau$ .
  - 3.3- Give, in terms of  $\tau$ , the minimum duration needed at the end of which the capacitor is practically totally discharged.
  - 3.4- Derive the expression of  $\ln u_C$ , the natural logarithm of  $u_C$ , in terms of  $E$ ,  $\tau$  and  $t$ .
  - 3.5- The diagram of figure 2 represents the variation



of  $\ln u_C$  as a function of time. Referring to the graph of figure 2, determine the value of  $R$ .