

Exercise Chapter 10 Part-A RC series circuit under constant and square signal


Charging of a capacitor:

Consider the adjacent circuit consist of:

- an ideal battery of electromotive force E ;
- a resistor of resistance R ;
- a capacitor of capacitance C , initially uncharged;
- a switch K .

Switch K is closed at $t_0 = 0$,

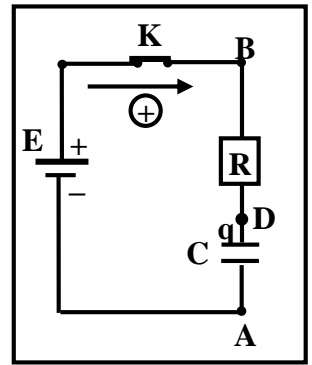At an instant t , the capacitor is charged by q and the circuit carries a current i .



- 1) Name the phenomenon that takes place.
- 2) Redraw the circuit showing the direction of the current.
- 3) An oscilloscope displays the voltage u_{BD} across the resistor on channel Y_1 , and the voltage $u_{DA} = u_C$ across the capacitor on channel Y_2 , the « INV » button of channel Y_2 being pressed. Why did we push in the knob «Inv»?
- 4) Redraw the circuit showing the connections of the oscilloscope displaying the voltages u_C and u_R .
- 5) Write the expression of the current i in terms of q .
- 6) Deduce the expression of i in terms of the capacitance C and the voltage u_C .
- 7) Derive the differential equation that governs the variation of the voltage, $u_{DA} = u_C$, across the capacitor.
- 8) Verify that the solution of this differential equation is $u_C = E \left(1 - e^{-\frac{t}{RC}} \right)$.

Or The solution of the obtained differential equation is of the form: $u_C = E \left(1 - e^{-\frac{t}{\tau}} \right)$, where τ is constant. Determine the expression of τ in terms of R and C .

Or The solution of this differential equation is: $u_C = D \left(1 - e^{-\frac{t}{\tau}} \right)$. Determine the expressions of the constants D and τ in terms of E , R and C .

Or The solution of this differential equation has the form of: $u_C = A + B e^{Dt}$. Determine the constants A , B and D in terms of E , R and C .

- 9) Determine, at the instant $t = 0$, the expression of the voltage u_C in terms of E .
- 10) Determine, at the instant $t = \tau$, the expression of the voltage u_C in terms of E .
- 11) Verify that the capacitor becomes practically fully charged at $t = 5 RC$.

12) Referring to the graph of $u_C = f(t)$ of the adjacent document: Determine the value of τ .

13) Deduce the value of the capacitance if the resistance $R = 200 \, \Omega$.

14) determine $\left. \frac{du_C}{dt} \right|_{t=0}$

From the differential equation of u_C

Or from the solution $u_C = E(1 - e^{-\frac{t}{\tau}})$.

Or Graphically

15) Determine the expression of the current i as a function of time t .

16) Determine, at the instant $t = 0$, the value of the current i .

or Determine the maximum value of the current I .

17) Determine, at the instant $t = \tau$, the expression of the current i in terms of E and R . deduce its value.

18) Deduce the value of the current i in steady state.

19) Sketch i as function of t .

20) Determine $\left. \frac{di}{dt} \right|_{t=0}$

from the solution i

Or Graphically

21) Determine the expression of the voltage across the resistor u_R as a function of time t .

Or if $u_C = E \left(1 - e^{-\frac{t}{RC}} \right)$. Deduce the expression of the voltage across the resistor u_R as a function of time t .

22) Determine, at the instant $t = 0$, the expression of the voltage across the resistor u_R .

or Determine the maximum value of the current u_R .

23) Determine, at the instant $t = \tau$, the expression of u_R in terms of E .

24) Deduce the value of the u_R in steady state.

25) Sketch u_R as function of t .

26) Determine $\left. \frac{du_R}{dt} \right|_{t=0}$

from the solution u_R

Or Graphically


27) If $u_C = E \left(1 - e^{-\frac{t}{RC}} \right)$. Determine the expression of the charge q as a function of time t .

28) Determine, at the instant $t = \tau$, the expression of q in terms of E and C .

29) Deduce the value of the u_R in steady state.

or Determine the maximum value of q .

30) Sketch q as function of t .

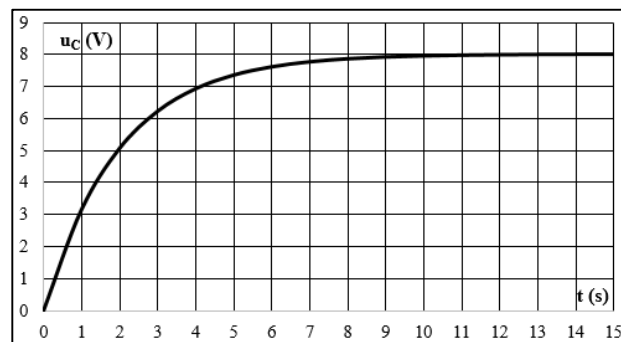

31) Determine $\frac{dq}{dt} \Big|_{t=0}$

from the solution q

Or Graphically

32) Derive the differential equation that governs the variation of the current i as function of time.

33) Derive the differential equation that governs the variation of the voltage u_R as function of time.

34) Derive the differential equation that governs the variation of the q as function of time.

35) A capacitor of capacitance 5000 μF is charged under a voltage of 12 V. Calculate the accumulated charge and the energy stored in this capacitor.

Discharging of a capacitor:

Consider the fully charged capacitor in the adjacent circuit, switch K is closed at new $t_0 = 0$,

At an instant t, the capacitor is charged by q and the circuit carries a current i.

36) Name the phenomenon that takes place.

37) Write the expression of the current i in terms of q.

38) Deduce the expression of i in terms of the capacitance C and the voltage u_C .

39) Derive the differential equation that governs the variation of the voltage, $u_{DA} = u_C$, across the capacitor.

40) Verify that the solution of this differential equation is $u_C = E e^{-\frac{t}{RC}}$.

Or The solution of the obtained differential equation is of the form: $u_C = E e^{-\frac{t}{\tau}}$, where τ is constant. Determine the expression of τ in terms of R and C.

41) Determine, at the instant $t = 0$, the expression of the voltage u_C in terms of E.

42) Determine, at the instant $t = \tau$, the expression of the voltage u_C in terms of E.

43) Verify that the capacitor becomes practically fully discharged at $t = 5 RC$.

44) Sketch u_C

45) determine $\frac{du_C}{dt} \Big|_{t=0}$ Graphically

46) Determine the expression of the current i as a function of time t.

47) Determine, at the instant $t = 0$, the value of the current i.

or Determine the maximum value of the current I.


48) Determine, at the instant $t = \tau$, the expression of the current i in terms of E and R.

49) Deduce the value of the current i in steady state.

50) Sketch i as function of t.

51) Determine $\frac{di}{dt} \Big|_{t=0}$

from the solution i

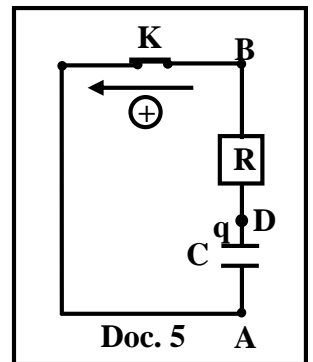

Or Graphically

52) Determine the expression of the voltage across the resistor u_R as a function of time t .

Or if $u_C = E \left(1 - e^{-\frac{t}{RC}}\right)$. Deduce the expression of the voltage across the resistor u_R as a function of time t .

53) Determine, at the instant $t = 0$, the expression of the voltage across the resistor u_R .

or Determine the maximum value of the current u_R .

54) Determine, at the instant $t = \tau$, the expression of u_R in terms of E .

55) Deduce the value of the u_R in steady state.

56) Sketch u_R as function of t .

57) Determine $\frac{du_R}{dt} \Big|_{t=0}$

from the solution u_R

Or Graphically

58) If $u_C = E e^{-\frac{t}{RC}}$. Determine the expression of the charge q as a function of time t .

59) Determine, at the instant $t = \tau$, the expression of q in terms of E and C .

60) Deduce the value of the u_R in steady state.



61) Sketch q as function of t .

62) Determine $\frac{dq}{dt} \Big|_{t=0}$ Graphically

63) Derive the differential equation that governs the variation of the current i as function of time.

64) Derive the differential equation that governs the variation of the voltage u_R as function of time.

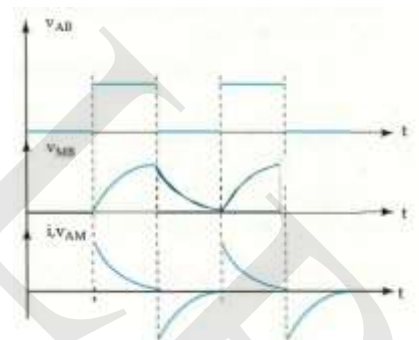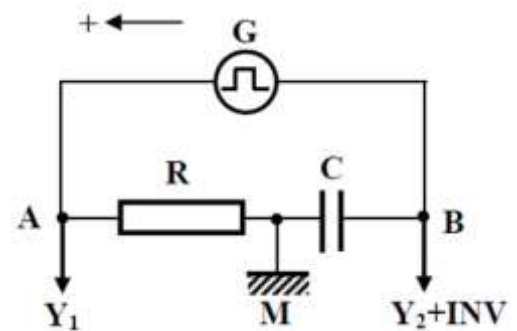65) Derive the differential equation that governs the variation of the q as function of time.



RC series circuit under square signal voltage

Consider the electric circuit, includes a resistor of resistance R , a capacitor of capacitance C , and a low frequency generator (LFG) delivering square signal voltage. Such that; Square signal: It is a periodic signal which takes a constant maximum value during one half-period, and is zero in the second half.

66) The waveform of u_{AM} represents the “image” of the current i . Why?

67) During discharging the curve u_R or i is negative. Why?

Charging of a capacitor:

Consider the adjacent circuit consist of:

- an ideal battery of electromotive force E ;
- a resistor of resistance R ;
- a capacitor of capacitance C , initially uncharged;
- a switch K .

Switch K is closed at $t_0 = 0$,

At an instant t , the capacitor is charged by q and the circuit carries a current i .

1) Name the phenomenon that takes place.

Ans: Charging of a capacitor

2) Redraw the circuit showing the direction of the current.

Ans: on the figure

3) An oscilloscope displays the voltage u_{BD} across the resistor on channel Y_1 , and the voltage $u_{DA} = u_C$ across the capacitor on channel Y_2 , the « INV » button of channel Y_2 being pressed. Why did we push in the knob «Inv»?

Ans: To display u_{DA} and not u_{AD}

4) Redraw the circuit showing the connections of the oscilloscope displaying the voltages u_C and u_R .

Ans: on the figure

5) Write the expression of the current i in terms of q .

Ans: $i = \frac{dq}{dt}$

6) Deduce the expression of i in terms of the capacitance C and the voltage u_C .

Ans: $q = Cu_C$ so $i = C \frac{du_C}{dt}$

7) Derive the differential equation that governs the variation of the voltage, $u_{DA} = u_C$, across the capacitor.

Ans: Apply law of addition of voltage $u_{BA} = u_{BD} + u_{DA}$, then $E = Ri + u_C$ where $i = \frac{dq}{dt} = C \frac{du_C}{dt}$

Then, $E = RC \frac{du_C}{dt} + u_C$

8) Verify that the solution of this differential equation is $u_C = E \left(1 - e^{-\frac{t}{RC}}\right)$.

Ans: $u_C = E \left(1 - e^{-\frac{t}{RC}}\right)$, then $\frac{du_C}{dt} = \frac{E}{RC} e^{-\frac{t}{RC}}$

$RC \frac{du_C}{dt} + u_C = RC \frac{E}{RC} e^{-\frac{t}{RC}} + E \left(1 - e^{-\frac{t}{RC}}\right) = E \left(e^{-\frac{t}{RC}}\right) + E - E \left(e^{-\frac{t}{RC}}\right) = E$ verified



Or The solution of the obtained differential equation is of the form: $u_C = E \left(1 - e^{-\frac{t}{\tau}}\right)$, where τ is constant. Determine the expression of τ in terms of R and C .

Ans: $u_C = E \left(1 - e^{-\frac{t}{\tau}}\right) = E - E e^{-\frac{t}{\tau}}$, then $\frac{du_C}{dt} = \frac{E}{\tau} e^{-\frac{t}{\tau}}$

Replacing u_C and $\frac{du_C}{dt}$ by their expressions in the differential equation, gives:

$E = RC \frac{E}{\tau} e^{-\frac{t}{\tau}} + E - E e^{-\frac{t}{\tau}}$, then $E e^{-\frac{t}{\tau}} \left(\frac{RC}{\tau} - 1\right) = 0$

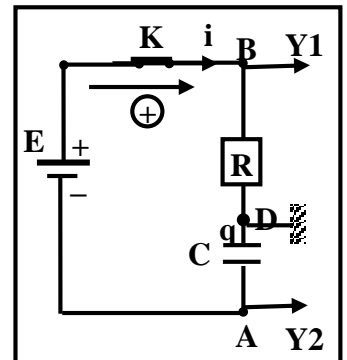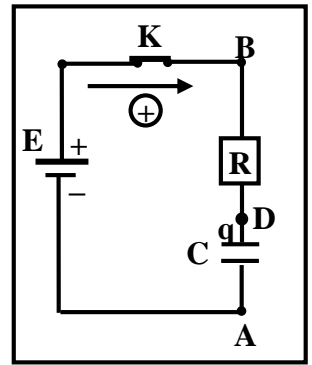$E e^{-\frac{t}{\tau}} = 0$ is rejected Then, $\left(\frac{RC}{\tau} - 1\right) = 0$; therefore, $\tau = RC$



Or The solution of this differential equation is: $u_C = D \left(1 - e^{-\frac{t}{\tau}} \right)$. Determine the expressions of the constants D and τ in terms of E , R and C .

Ans: $u_C = D \left(1 - e^{-\frac{t}{\tau}} \right)$ then $\frac{du_C}{dt} = -D \left(-\frac{1}{\tau} \right) e^{-\frac{t}{\tau}} = \frac{D}{\tau} e^{-\frac{t}{\tau}}$

Replace u_C and $\frac{du_C}{dt}$ by their expressions in the differential equation.

We get: $RC \frac{D}{\tau} e^{-\frac{t}{\tau}} + D - D e^{-\frac{t}{\tau}} = E \quad \forall t$

$D \left(\frac{RC}{\tau} - 1 \right) e^{-\frac{t}{\tau}} + D - E = 0 \quad \forall t$

Comparing, we get: $D - E = 0$ then $D = E$

$\left(\frac{RC}{\tau} - 1 \right) = 0$ then $\tau = RC$

Or The solution of this differential equation has the form of: $u_C = A + B e^{Dt}$. Determine the constants A , B and D in terms of E , R and C .

Ans: $u_C = A + B e^{Dt}$, so $\frac{du_C}{dt} = B D e^{Dt}$, substitute in the differential equation

$B D e^{Dt} + \frac{A + B e^{Dt}}{RC} = \frac{E}{RC}$, then $RC B D e^{Dt} + A + B e^{Dt} = E$

$B e^{Dt} (RC D + 1) + A = E$.

$A = E$; and $B e^{Dt} (RC D + 1) = 0$. But $B e^{Dt} = 0$ is rejected,

then $(RC D + 1) = 0$, thus $D = -\frac{1}{RC}$.

At $t_0 = 0$, $u_C = 0 = A + B e^{Dt}$, so $0 = A + B$, then $B = -A$, therefore $B = -E$.

9) Determine, at the instant $t = 0$, the expression of the voltage u_C in terms of E .

Ans: At $t = 0$; $u_C = E(1 - e^0) = E(1 - 1) = 0$

10) Determine, at the instant $t = \tau$, the expression of the voltage u_C in terms of E .

Ans: At $t = \tau$; $u_C = E \left(1 - e^{-\frac{\tau}{\tau}} \right) = E(1 - e^{-1}) \approx 0,63E$

11) Verify that the capacitor becomes practically fully charged at $t = 5 RC$.

At $t = 5 RC$: $u_C = E \left(1 - e^{-\frac{5 RC}{RC}} \right) = E(1 - e^{-5})$, then $u_C = 0.99 E$. Therefore, the capacitor becomes practically fully charged at $t = 5 RC$.

12) Referring to the graph of $u_C = f(t)$ of the adjacent document: Determine the value of τ .


Ans: At $t = \tau$;

$u_C = 0.63E = 0.63 \times 8 = 5.04 \text{ V} \approx 5 \text{ V}$

from the graph we get: $\tau = 2 \text{ s}$

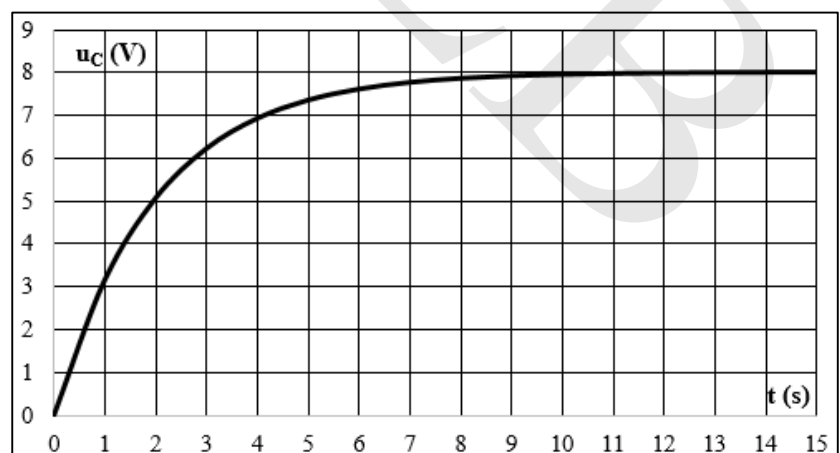13) Deduce the value of the value of the capacitance if the resistance $R = 200 \Omega$.

Ans: $\tau = RC$ then $C = \frac{\tau}{R} = \frac{2}{200} = 10^{-2} \text{ F}$



14) determine $\frac{du_C}{dt} \Big|_{t=0}$

From the differential equation of u_C


Ans: $\frac{du_C}{dt} + \frac{u_C}{RC} = \frac{E}{RC}$ at $t=0$, $u_C = 0$ so $\frac{du_C}{dt} \Big|_{t=0} = \frac{E}{RC}$

Or from the solution $u_C = E(1 - e^{-\frac{t}{\tau}})$.

Ans: $u_C = E(1 - e^{-\frac{t}{\tau}})$ then $\frac{du_C}{dt} = \frac{E}{\tau} e^{-\frac{t}{\tau}}$ So $\frac{du_C}{dt} \Big|_{t=0} = \frac{E}{\tau} e^0 = \frac{E}{RC}$

Or Graphically

Ans: $\frac{du_C}{dt} \Big|_{t=0} = \text{slope of the tangent to the curve at } (t=0) = \tan \alpha = \frac{E}{\tau} = \frac{E}{RC}$

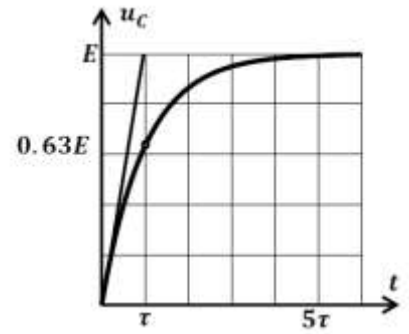

15) Determine the expression of the current i as a function of time t .

Ans: $i = C \frac{du_C}{dt} = C \frac{E}{\tau} e^{-\frac{t}{\tau}} = C \frac{E}{RC} e^{-\frac{t}{\tau}} = \frac{E}{R} e^{-\frac{t}{\tau}}$

16) Determine, at the instant $t = 0$, the value of the current i .

or Determine the maximum value of the current I .

Ans: At $t = 0$; $i = \frac{E}{R} e^0 = \frac{E}{R} = \frac{8}{200} = 0.04 \text{ A}$ then $I = 0.04 \text{ A}$

17) Determine, at the instant $t = \tau$, the expression of the current i in terms of E and R . deduce its value.

Ans: At $t = \tau$; $i = \frac{E}{R} e^{-\tau/\tau} = \frac{E}{R} e^{-1} = 0.367 \frac{E}{R}$ then $i = 0.0147 \text{ A}$

18) Deduce the value of the current i in steady state.

Ans: at steady state: $t = \infty$; $i = \frac{E}{R} e^{-\frac{\infty}{\tau}} = \frac{E}{R} \times 0 = 0 \text{ A}$

19) Sketch i as function of t .

Ans: figure


20) Determine $\frac{di}{dt} \Big|_{t=0}$

from the solution i

Ans: $i = I_m e^{-\frac{t}{\tau}}$ then $\frac{di}{dt} = -\frac{I_m}{\tau} e^{-\frac{t}{\tau}}$ So $\frac{di}{dt} \Big|_{t=0} = -\frac{I_m}{\tau} e^0 = -\frac{I_m}{RC} = -\frac{E}{R^2C}$

Or Graphically

Ans: $\frac{di}{dt} \Big|_{t=0} = \text{slope of the tangent to the curve at } (t=0) = \tan \alpha = -\frac{E/R}{\tau} = -\frac{E}{R^2C}$

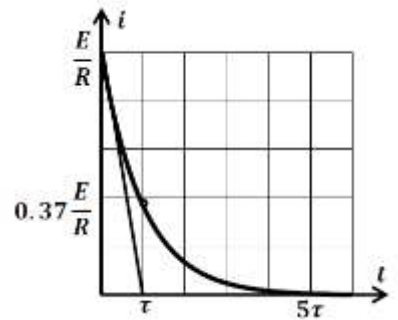

21) Determine the expression of the voltage across the resistor u_R as a function of time t .

Ans: $u_R = Ri = R \frac{E}{R} e^{-\frac{t}{RC}} = E e^{-\frac{t}{RC}}$

Or if $u_C = E(1 - e^{-\frac{t}{RC}})$. Deduce the expression of the voltage across the resistor u_R as a function of time t .

Ans: $u_R + u_C = E$ then $u_R = E - u_C = E - E(1 - e^{-\frac{t}{RC}}) = E e^{-\frac{t}{RC}}$

22) Determine, at the instant $t = 0$, the expression of the voltage across the resistor u_R .

or Determine the maximum value of the current u_R .

Ans: At $t = 0$; $u_R = E e^{-\frac{t}{RC}} = E e^0 = E$

23) Determine, at the instant $t = \tau$, the expression of u_R in terms of E .

Ans: At $t = \tau$; $u_R = E e^{-1} = 0.367 E$

24) Deduce the value of the u_R in steady state.

Ans: at steady state: $t = \infty$; $u_R = E e^{-\frac{\infty}{RC}} = E \times 0 = 0 \text{ V}$

25) Sketch u_R as function of t .


Ans: figure

26) Determine $\frac{du_R}{dt} \Big|_{t=0}$
from the solution u_R

Ans: $u_R = E e^{-\frac{t}{\tau}}$ then $\frac{du_R}{dt} = -\frac{E}{\tau} e^{-\frac{t}{\tau}}$ So $\frac{du_R}{dt} \Big|_{t=0} = -\frac{E}{\tau} e^0 = -\frac{E}{\tau}$

Or Graphically

Ans: $\frac{du_R}{dt} \Big|_{t=0}$ = slope of the tangent to the curve at $(t=0) = \tan \alpha = -\frac{E}{\tau} = -\frac{E}{RC}$

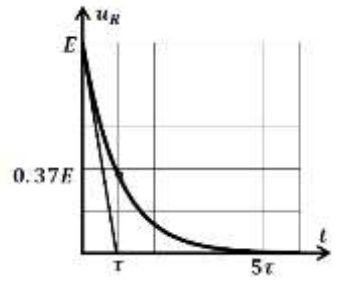

27) If $u_C = E \left(1 - e^{-\frac{t}{RC}}\right)$. Determine the expression of the charge q as a function of time t .

Ans: $q = Cu_C = CE(1 - e^{-\frac{t}{RC}})$

28) Determine, at the instant $t = \tau$, the expression of q in terms of E and C .

Ans: At $t = \tau$; $q = Cu_C = CE(1 - e^{-1}) = 0.63 CE$

29) Deduce the value of the u_R in steady state.

or Determine the maximum value of q .

Ans: at steady state: $t = \infty$; $q = CE(1 - e^{-\infty}) = CE(1 - 0) = CE$ then $Q_m = CE$.

30) Sketch q as function of t .


Ans: figure

31) Determine $\frac{dq}{dt} \Big|_{t=0}$
from the solution q

Ans: $q = Q_m(1 - e^{-\frac{t}{\tau}})$ then $\frac{dq}{dt} = \frac{Q_m}{\tau} e^{-\frac{t}{\tau}}$ So $\frac{dq}{dt} \Big|_{t=0} = \frac{Q_m}{\tau} e^0 = \frac{Q_m}{\tau} = \frac{E}{R}$

Or Graphically

Ans: $\frac{dq}{dt} \Big|_{t=0}$ = slope of the tangent to the curve at $(t=0) = \tan \alpha = \frac{CE}{\tau} = \frac{E}{R}$

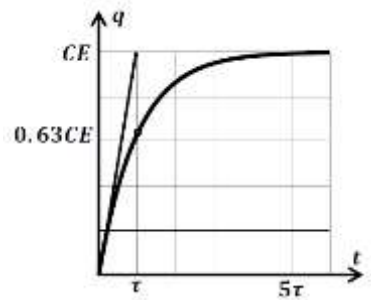

32) Derive the differential equation that governs the variation of the current i as function of time.

Ans: Apply Law of addition of voltages: $u_R + u_C = u_G$ where $u_R = Ri$ and $q = Cu_C$

$Ri + \frac{q}{C} = E$ where $i = \frac{dq}{dt}$ Derive with respect to time $R \frac{di}{dt} + \frac{1}{C} \frac{dq}{dt} = 0$

$R \frac{di}{dt} + \frac{i}{C} = 0$ then $\frac{di}{dt} + \frac{i}{RC} = 0$

33) Derive the differential equation that governs the variation of the voltage u_R as function of time.

Ans: Law of addition of voltages: $u_R + u_C = u_G$ where $q = Cu_C$

$u_R + \frac{q}{C} = E$ where $i = \frac{dq}{dt}$ Derive with respect to time

$\frac{du_R}{dt} + \frac{1}{C} \frac{dq}{dt} = 0$ then $\frac{du_R}{dt} + \frac{i}{C} = 0$ then $\frac{du_R}{dt} + \frac{Ri}{RC} = 0$ so $\frac{du_R}{dt} + \frac{u_R}{RC} = 0$

34) Derive the differential equation that governs the variation of the q as function of time.

Ans: Law of addition of voltages: $u_R + u_C = u_G$

$Ri + u_C = E$ Where $i = \frac{dq}{dt}$ and $q = Cu_C$ then $R \frac{dq}{dt} + \frac{q}{C} = E$ so $\frac{dq}{dt} + \frac{q}{RC} = \frac{E}{R}$

35) A capacitor of capacitance $5000 \mu F$ is charged under a voltage of $12 V$. Calculate the accumulated charge and the energy stored in this capacitor.

Ans: Accumulated charge: $Q = CV = 5000 \times 10^{-6} \times 12 = 6 \times 10^{-2} C$.

Stored energy: $W = \frac{1}{2} QV = \frac{1}{2} \times (6 \times 10^{-2}) \times 12 = 36 \times 10^{-2} J$.

Discharging of a capacitor:

Consider the fully charged capacitor in the adjacent circuit, switch K is closed at new $t_0 = 0$,

At an instant t , the capacitor is charged by q and the circuit carries a current i .

36) Name the phenomenon that takes place.

Ans: discharging of a capacitor

37) Write the expression of the current i in terms of q .

Ans: $i = -\frac{dq}{dt}$

38) Deduce the expression of i in terms of the capacitance C and the voltage u_C .

Ans: $q = Cu_C$ so $i = -C \frac{du_C}{dt}$

39) Derive the differential equation that governs the variation of the voltage, $u_{DA} = u_C$, across the capacitor.

Ans: Apply law of addition of voltage $u_{BA} = u_{BD} + u_{DA}$, then $0 = -Ri + u_C$ where $i = -C \frac{du_C}{dt}$

Then, $RC \frac{du_C}{dt} + u_C = 0$

40) Verify that the solution of this differential equation is $u_C = E e^{-\frac{t}{RC}}$.

Ans: $u_C = E e^{-\frac{t}{RC}}$ then $\frac{du_C}{dt} = -\frac{E}{RC} e^{-\frac{t}{RC}}$

$$RC \frac{du_C}{dt} + u_C = -RC \frac{E}{RC} e^{-\frac{t}{RC}} + E e^{-\frac{t}{RC}} = -E \left(e^{-\frac{t}{RC}} \right) + E \left(e^{-\frac{t}{RC}} \right) = 0 \text{ verified}$$

Or The solution of the obtained differential equation is of the form: $u_C = E e^{-\frac{t}{\tau}}$, where τ is constant. Determine the expression of τ in terms of R and C .

Ans: $u_C = E e^{-\frac{t}{\tau}}$, then $\frac{du_C}{dt} = -\frac{E}{\tau} e^{-\frac{t}{\tau}}$

Replacing u_C and $\frac{du_C}{dt}$ by their expressions in the differential equation, gives:

$$-RC \frac{E}{\tau} e^{-\frac{t}{\tau}} + E e^{-\frac{t}{\tau}} = 0, \text{ then } E e^{-\frac{t}{\tau}} \left(\frac{RC}{\tau} - 1 \right) = 0$$

$E e^{-\frac{t}{\tau}} = 0$ is rejected Then, $\left(\frac{RC}{\tau} - 1 \right) = 0$; therefore, $\tau = RC$

41) Determine, at the instant $t = 0$, the expression of the voltage u_C in terms of E .

Ans: At $t = 0$; $u_C = E(e^0) = E(1) = E$

42) Determine, at the instant $t = \tau$, the expression of the voltage u_C in terms of E .

Ans: At $t = \tau$; $u_C = E \left(e^{-\frac{\tau}{\tau}} \right) = E(e^{-1}) \approx 0,37E$

43) Verify that the capacitor becomes practically fully discharged at $t = 5 RC$.



At $t = 5 RC$: $u_C = E \left(e^{-\frac{5 RC}{RC}} \right) = E(e^{-5})$, then $u_C = 0.006 E$. Therefore, the capacitor becomes practically fully discharged at $t = 5 RC$.

44) Sketch u_C

Ans: the figure

45) determine $\left. \frac{du_C}{dt} \right|_{t=0}$ Graphically

Ans: $\left. \frac{du_C}{dt} \right|_{t=0} = \text{slope of the tangent to the curve at } (t=0) = \tan \alpha = -\frac{E}{\tau} = -\frac{E}{RC}$

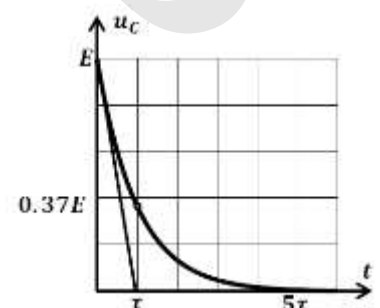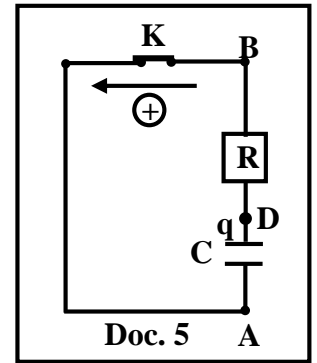

46) Determine the expression of the current i as a function of time t .

$$\text{Ans: } i = -C \frac{du_C}{dt} = -C \frac{E}{\tau} e^{-\frac{t}{\tau}} = -C \frac{E}{RC} e^{-\frac{t}{\tau}} = -\frac{E}{R} e^{-\frac{t}{\tau}}$$

47) Determine, at the instant $t = 0$, the value of the current i .

or Determine the maximum value of the current I .

$$\text{Ans: At } t = 0 ; i = \frac{E}{R} e^0 = \frac{E}{R}$$

48) Determine, at the instant $t = \tau$, the expression of the current i in terms of E and R .

$$\text{Ans: At } t = \tau ; i = \frac{E}{R} e^{-\tau/\tau} = \frac{E}{R} e^{-1} = 0.367 \frac{E}{R}$$

49) Deduce the value of the current i in steady state.

$$\text{Ans: at steady state: } t = \infty ; i = \frac{E}{R} e^{-\frac{\infty}{\tau}} = \frac{E}{R} \times 0 = 0 \text{ A}$$

50) Sketch i as function of t .


Ans: figure

51) Determine $\left. \frac{di}{dt} \right|_{t=0}$
from the solution i

$$\text{Ans: } i = I_m e^{-\frac{t}{\tau}} \text{ then } \frac{di}{dt} = -\frac{I_m}{\tau} e^{-\frac{t}{\tau}} \text{ So } \left. \frac{di}{dt} \right|_{t=0} = -\frac{I_m}{\tau} e^0 = -\frac{I_m}{\tau} = -\frac{E}{R^2 C}$$

Or Graphically

$$\text{Ans: } \left. \frac{di}{dt} \right|_{t=0} = \text{slope of the tangent to the curve at } (t=0) = \tan \alpha = -\frac{E/R}{\tau} = -\frac{E}{R^2 C}$$

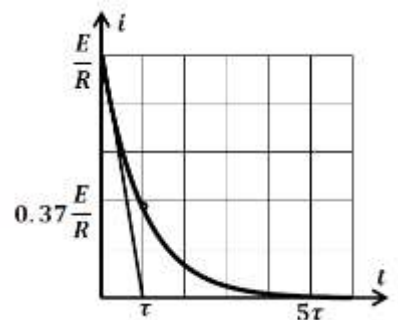

52) Determine the expression of the voltage across the resistor u_R as a function of time t .

$$\text{Ans: } u_R = Ri = R \frac{E}{R} e^{-\frac{t}{RC}} = E e^{-\frac{t}{RC}}$$

Or if $u_C = E \left(1 - e^{-\frac{t}{RC}}\right)$. Deduce the expression of the voltage across the resistor u_R as a function of time t .

$$\text{Ans: } u_R + u_C = E \text{ then } u_R = E - u_C = E - E \left(1 - e^{-\frac{t}{RC}}\right) = E e^{-\frac{t}{RC}}$$

53) Determine, at the instant $t = 0$, the expression of the voltage across the resistor u_R .

or Determine the maximum value of the current u_R .

$$\text{Ans: At } t = 0 ; u_R = E e^{-\frac{t}{RC}} = E e^0 = E$$

54) Determine, at the instant $t = \tau$, the expression of u_R in terms of E .

$$\text{Ans: At } t = \tau ; u_R = E e^{-1} = 0.367 E$$

55) Deduce the value of the u_R in steady state.

$$\text{Ans: at steady state: } t = \infty ; u_R = E e^{-\frac{\infty}{RC}} = E \times 0 = 0 \text{ V}$$

56) Sketch u_R as function of t .


Ans: figure

57) Determine $\left. \frac{du_R}{dt} \right|_{t=0}$
from the solution u_R

$$\text{Ans: } u_R = E e^{-\frac{t}{\tau}} \text{ then } \frac{du_R}{dt} = -\frac{E}{\tau} e^{-\frac{t}{\tau}} \text{ So } \left. \frac{du_R}{dt} \right|_{t=0} = -\frac{E}{\tau} e^0 = -\frac{E}{RC}$$

Or Graphically

$$\text{Ans: } \left. \frac{du_R}{dt} \right|_{t=0} = \text{slope of the tangent to the curve at } (t=0) = \tan \alpha = -\frac{E}{\tau} = -\frac{E}{RC}$$

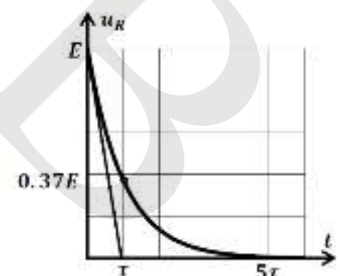

58) If $u_C = E e^{-\frac{t}{RC}}$. Determine the expression of the charge q as a function of time t .

$$\text{Ans: } q = Cu_C = CE(1 - e^{-\frac{t}{RC}})$$

59) Determine, at the instant $t = \tau$, the expression of q in terms of E and C .

$$\text{Ans: At } t = \tau ; q = Cu_C = CE(e^{-1}) = 0.37 CE$$

60) Deduce the value of the u_R in steady state.


Ans: at steady state: $t = \infty$; $q = CE(e^{-\infty}) = CE(0) = 0$ then Q_m

61) Sketch q as function of t .

Ans: figure

62) Determine $\left. \frac{dq}{dt} \right|_{t=0}$ Graphically

Ans: $\left. \frac{dq}{dt} \right|_{t=0} = \text{slope of the tangent to the curve at } (t=0) = \tan \alpha = -\frac{CE}{\tau} = -\frac{E}{R}$

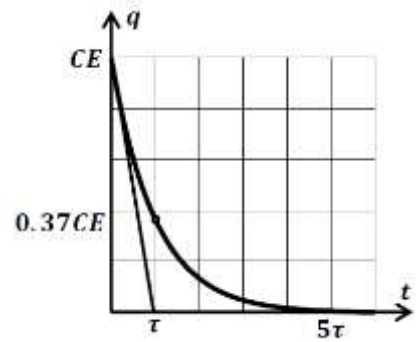

63) Derive the differential equation that governs the variation of the current i as function of time.

Ans: Law of addition of voltages: $u_{AB(R)} + u_{BA(C)} = 0$ where $u_{BA(C)} = -u_C$

$u_R - u_C = 0$ where $u_R = Ri$ and $q = Cu_C$ then $Ri - \frac{q}{C} = 0$

$Ri = \frac{q}{C}$ Derive with respect to time $R \frac{di}{dt} = \frac{1}{C} \frac{dq}{dt}$ where $i = -\frac{dq}{dt}$

$R \frac{di}{dt} + \frac{i}{C} = 0$ so $\frac{di}{dt} + \frac{i}{RC} = 0$

64) Derive the differential equation that governs the variation of the voltage u_R as function of time.

Ans: Law of addition of voltages: $u_{AB(R)} + u_{BA(C)} = 0$ where $u_{BA(C)} = -u_C$

$u_R - u_C = 0$ where $q = Cu_C$ then $u_R - \frac{q}{C} = 0$

$u_R = \frac{q}{C}$ Derive with respect to time $\frac{du_R}{dt} = \frac{1}{C} \frac{dq}{dt}$ Where $i = -\frac{dq}{dt}$

$\frac{du_R}{dt} + \frac{i}{C} = 0$ then $\frac{du_R}{dt} + \frac{Ri}{RC} = 0$ so $\frac{du_R}{dt} + \frac{u_R}{RC} = 0$

65) Derive the differential equation that governs the variation of the q as function of time.


Ans: Law of addition of voltages:

$u_{AB(R)} + u_{BA(C)} = 0$ where $u_R = Ri$ and $u_{BA(C)} = -u_C$ then $Ri - u_C = 0$ Where $i = -\frac{dq}{dt}$ and $q = Cu_C$

$R \frac{dq}{dt} - \frac{q}{C} = 0$ so $R \frac{dq}{dt} + \frac{q}{C} = 0$

RC series circuit under square signal voltage

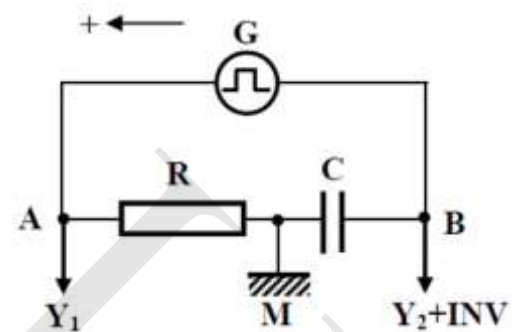Consider the electric circuit, includes a resistor of resistance R , a capacitor of capacitance C , and a low frequency generator (LFG) delivering square signal voltage. Such that; Square signal: It is a periodic signal which takes a constant maximum value during one half-period, and is zero in the second half.



66) The waveform of u_{AM} represents the "image" of the current i . Why?

Ans: $u_{AM} = Ri$ then $i = u_{AM}/R$ so the curve of u_{AM} represents the image of i .

67) During discharging the curve u_R or i is negative. Why?

Ans: During discharging:

$u_{AM(R)} + u_{MB(C)} = 0$

$u_{AM(R)} = -u_{MB(C)}$

